

Roll No.

--	--	--	--	--	--	--	--	--	--

**SHAMBHUNATH INSTITUTE OF ENGINEERING AND TECHNOLOGY**

**Subject : Digital System Design      Subject Code : KEC302**

**B.Tech. 3<sup>rd</sup> SEMESTER**

**FIRST SESSIONAL EXAMINATION, ODD SEMESTER, (2019-2020)**

**Branch : Electronics & Communication Engineering**

**Time –1hr 30 min**

**Maximum Marks – 30**

**SECTION - A**

**Q-1) Attempt ALL parts-**

**(5\*1 = 05)**

- Perform the following conversions : (A)  $(101000100111)_2 = ( ? )_{10}$       (B)  $(511)_{10} = ( ? )_8$
- State De Morgan's theorem.
- How many 3:8 line decoder with enable input are required to construct 6:64 line decoder without using any other logic?
- Explain magnitude comparator?
- Differentiate between combinational and sequential circuits.

**SECTION - B**

**Q 2) Attempt any TWO parts from this section.**

**(2\*5 = 10)**

- Determine the POS expression using K-map.

$$f = x'z' + wyz + w'y'z' + x'y$$

- Implement a full subtractor using two 4:1 Multiplexer.
- Design a 4 bit parallel adder circuit by using full adder.
- Explain the operation of a SR flip-flop.

**SECTION - C**

**3. Attempt any ONE part of the following :**

**(1\*5 = 5)**

- Minimized the expression and Realize the expression using NAND gate only.  
 $F(A,B,C,D,E) = \sum m (1, 3, 4, 5, 11, 12, 14, 16, 20, 21, 30)$
- Minimize the following function using Quine-McClusky method:

$$F(A,B,C,D) = \sum m(0,3,5,6,7,10,12,13) + d(2,9,15)$$

**4. Attempt any ONE part of the following :**


**(1\*5 = 5)**

- Implement the following function using a 3 to 8 line decoder  $F_1 = \sum (3,5,6,7)$  and  $F_2 = \sum (1,2,4,7)$
- Using 8:1 MUX with A as input line, realize the following function with multiplexer.  
 $F(A,B,C,D) = \sum m (0,1,2,4,6,9,12,14)$

**5. Attempt any ONE part of the following :**

 **(1\*5 = 5)**

- Analyze the logic circuit shown below and determine the output Y.



- Design an 8-bit adder/subtractor using ALU 74181s in cascade. Show how it works if A=97 and B=29.

**Solution Subject : Digital System Design    Subject Code : KEC302**  
**B.Tech. 3<sup>rd</sup> SEMESTER**  
**FIRST SESSIONAL EXAMINATION, ODD SEMESTER, (2019-2020)**  
**Branch : Electronics & Communication Engineering**

**Time –1hr 30 min**

**Maximum Marks – 30**

**SECTION - A**


**Q-1) ANSWERS**

**(5\*1 = 05)**

- a) **ANS :** conversions : (A)  $(101000100111)_2 = (\underline{2599})_{10}$     (B)  $(511)_{10} = (\underline{777})_8$
- b) **ANS :** The complement of the product of two or more variables is equal to the sum of the complements of the variables.

$$\overline{A + B} = \overline{A} \cdot \overline{B} \quad \text{OR} \quad \overline{A \cdot B} = \overline{A} + \overline{B}$$

 - c) **ANS : NINE** 3:8 line decoder with enable input are required to construct 6:64 line decoder without using any other logic.
- d) **ANS :** A magnitude comparator is a combinational circuit that compares two numbers A & B to determine whether:  $A > B$ ,    or  $A = B$ ,    or  $A < B$



- e) **ANS :**

A combinational system (device) is a digital system in which the value of the output at any instant depends only on the value of the input at that same instant (and not on previous values).


A sequential circuit is a circuit with memory. A sequential circuit is said to be synchronous if the internal state of the machine changes at specific instants of time as governed by a clock.

**SECTION - B**

**Q 2) Attempt any TWO parts from this section.**

**(2\*5 = 10)**

 
- a. **ANS :** The POS expression using K-map.



$$f = (y + z')(w' + x' + z)(w + x' + y')$$


b. ANS : Full subtractor using two 4:1 Multiplexer.

Truth Table

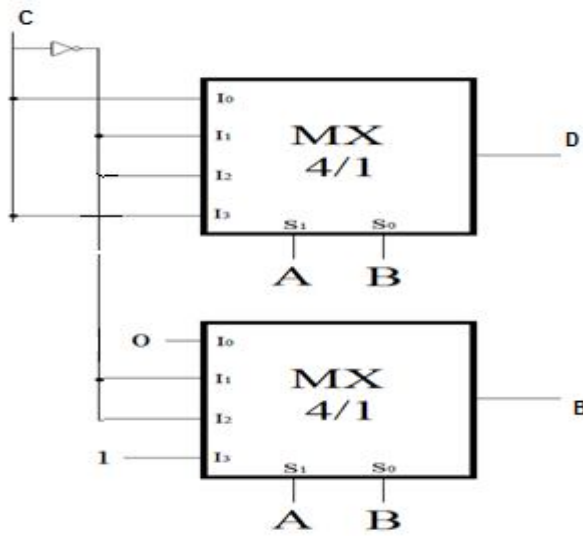

C	B	A	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 c. ANS : A 4 bit parallel adder circuit by using full adder.



e. ANS : operation of a SR flip-flop.

From the diagram it is evident that the flip flop has mainly four states. They are


**S=1, R=0—Q=1, Q'=0** This state is also called the SET state.

**S=0, R=1—Q=0, Q'=1** This state is known as the RESET state.

**S=0, R=0—Q & Q' = previous state.**

 **S=1, R=1—Q=0, Q'=0 [Invalid]**

This is an invalid state because the values of both Q and Q' are 0. They are supposed to be compliments of each other. Normally, this state must be avoided.



(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(after S=1, R=0)  
(after S=0, R=1)

## SECTION - C

3. Attempt any ONE part of the following :

(1\*5 = 5)

a)  $F = B'CD' + A'BCE' + BCDE' + A'C'DE + AB'D'E' + A'B'C'E$

b) ANS : Quine-McClusky method:

For Minterms:	Minterm ID	W	X	Y	Z
	0	0	0	0	0
	3	0	0	1	1
	5	0	1	0	1
	6	0	1	1	0
	7	0	1	1	1
	10	1	0	1	0
	12	1	1	0	0
	13	1	1	0	1

For don't cares:	Minterm ID	W	X	Y	Z
	2	0	0	1	0
	9	1	0	0	1
	15	1	1	1	1

Groups	Minterm ID	W	X	Y	Z	Merge Mark
G0	0	0	0	0	0	<input type="checkbox"/>
G1	2	0	0	1	0	<input type="checkbox"/>
G2	3	0	0	1	1	<input type="checkbox"/>
	5	0	1	0	1	<input type="checkbox"/>
	6	0	1	1	0	<input type="checkbox"/>
	9	1	0	0	1	<input type="checkbox"/>
	10	1	0	1	0	<input type="checkbox"/>
G3	7	0	1	1	1	<input type="checkbox"/>
	13	1	1	0	1	<input type="checkbox"/>
	15	1	1	1	1	<input type="checkbox"/>

Groups	Minterm ID	W	X	Y	Z	Merge Mark
G0'	0, 2	0	0	d	0	<input type="checkbox"/>
G1'	2, 3	0	0	1	d	<input type="checkbox"/>
	2, 6	0	d	1	0	<input type="checkbox"/>
	2, 10	d	0	1	0	<input type="checkbox"/>
	3, 7	0	d	1	1	<input type="checkbox"/>
G2'	5, 7	0	1	d	1	<input type="checkbox"/>
	6, 7	0	1	1	d	<input type="checkbox"/>
	5, 13	d	1	0	1	<input type="checkbox"/>
	9, 13	1	d	0	1	<input type="checkbox"/>
	12, 13	1	1	0	d	<input type="checkbox"/>
G3'	7, 15	d	1	1	1	<input type="checkbox"/>
	13, 15	1	1	d	1	<input type="checkbox"/>

Groups	Minterm ID	W	X	Y	Z	Merge Mark
G0''	0, 2	0	0	d	0	<input type="checkbox"/>
G1''	2, 3, 6, 7	0	d	1	d	<input type="checkbox"/>
	2, 10	d	0	1	0	<input type="checkbox"/>
	3, 7	0	d	1	1	<input type="checkbox"/>
G2''	5, 7	0	1	d	1	<input type="checkbox"/>
	6, 7	0	1	1	d	<input type="checkbox"/>
	5, 13	d	1	0	1	<input type="checkbox"/>
	9, 13	1	d	0	1	<input type="checkbox"/>
	12, 13	1	1	0	d	<input type="checkbox"/>
G3''	7, 15	d	1	1	1	<input type="checkbox"/>
	13, 15	1	1	d	1	<input type="checkbox"/>

Groups	Minterm ID	W	X	Y	Z	Merge Mark
G0''	0, 2	0	0	d	0	<input type="checkbox"/>
G1''	2, 3, 6, 7	0	d	1	d	<input type="checkbox"/>
	2, 10	d	0	1	0	<input type="checkbox"/>
G2''	5, 7, 13, 15	d	1	d	1	<input type="checkbox"/>
	9, 13	1	d	0	1	<input type="checkbox"/>
	12, 13	1	1	0	d	<input type="checkbox"/>
	7, 15	d	1	1	1	<input type="checkbox"/>

Groups	Minterm ID	W	X	Y	Z	Merge Mark
G0''	0, 2	0	0	d	0	<input type="checkbox"/>
G1''	2, 3, 6, 7	0	d	1	d	<input type="checkbox"/>
	2, 10	d	0	1	0	<input type="checkbox"/>
G2''	5, 7, 13, 15	d	1	d	1	<input type="checkbox"/>
	9, 13	1	d	0	1	<input type="checkbox"/>
	12, 13	1	1	0	d	<input type="checkbox"/>
	7, 15	d	1	1	1	<input type="checkbox"/>


Minterm ID	$\bar{W}\bar{X}\bar{Z}$	$\bar{W}Y$	$\bar{X}Y\bar{Z}$	$XZ$	$WXY$	$W\bar{Y}Z$
0	1					
3		1				
5				1		
6		1				
7		1		1		
10			1			
12					1	
13				1	1	1

$$F(W, X, Y, Z) = \bar{W}\bar{X}\bar{Z} + \bar{W}Y + \bar{X}Y\bar{Z} + XZ + WXY$$

4. Attempt any ONE part of the following :

(1\*5 = 5)

 
c) Implement the function using a 3 to 8 line decoder.  $F_1(x,y,z) = \sum(3,5,6,7)$  and  $F_2(x,y,z) = \sum(1,2,4,7)$



d) Using 8:1 MUX with A as input line, realize the following function with multiplexer.

$$F(A,B,C,D) = \sum m(0,1,2,4,6,9,12,14)$$


	$I_0$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$
$\bar{A}$	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	$\bar{A}$	1	$\bar{A}$	0	1	0	1	0

 

5. Attempt any ONE part of the following :

(1\*5 = 5)

 a) Analyze the logic circuit shown below and determine the output Y.



b) **Solution :** For designing an 8-bit adder/subtractor, two 74181 ICs are to be cascaded.

- The least-significant four bits of A & B are applied at the A & B inputs of the LSB 74181 and the most-significant four bits of A & B are applied at the A & B inputs of the MSB 74181.
- The carry-out of the least-significant 74181 is connected to the carry-in of the most-significant 74181.
- The 8-bit output will be available on F outputs.
- The select lines of both the 74181s are connected together.
- Addition is performed with M=0 and S=1011, and
- subtraction is performed with M=0 and S = 0110.
- Connect  $C_n$  of least-significant 74181 to 1 for addition and 0 for subtraction.

(a)  $A=97 = 01100001$        $B=29 = 00011101$

Mode control M	Select inputs $S_3S_2S_1S_0$	least-significant ALU					Most-significant ALU					Output	Remark
		Inputs			Outputs		Inputs			Outputs			
		$A_L$	$B_L$	$C_{in}$	$S_L$	$C_{n+4}$	$A_H$	$B_H$	$C_{in}$	$S_H$	$C_{n+4}$		
0	1001	0001	1101	1	1110	1	0110	0001	1	0111	1	01111110	$(126)_{10}$
0	0110	0001	1101	0	0100	1	0110	0001	1	0100	0	01000100	$(68)_{10}$