

SHAMBHUNATH INSTITUTE OF ENGINEERING & TECHNOLOGY

Important Theory Questions for Unit-3

Sub- Basic Electrical Engineering (NEE-101)

- Q (1). Derive relationship between line and phase voltage and current in 3- phase balanced star connected load.
- Q (2). Show that $V_L = \sqrt{3} V_P$ for three-phase balanced star connected load.
- Q (3). Show that $I_L = \sqrt{3} I_P$ for three-phase balanced delta connected load.
- Q (4). Derive relationship between line and phase voltage and current in 3- phase balanced delta connected load.
- Q (5). Explain power measurement by two wattmeter method.
- Q (6). Show that $\cos \phi = \cos \tan^{-1} \left[\frac{W_1 - W_2}{W_1 + W_2} \right]$ for power measurement by two wattmeter method.
- Q (7). Describe the working and construction of PMMC type instrument or voltmeter or ammeter, with neat and clean diagram. Also show that deflection of pointer (θ) $\propto I$. Mention its merits and demerits.
- Q (8). Describe the working and construction of Electrodynamic or Dynamometer type wattmeter. Also show that deflection of pointer indicates average power.
- Q (9). Explain the working and construction of repulsion type moving iron instrument or ammeter or voltmeter with neat and clean diagram. Mention its merits and demerits. Also show that pointer deflection (θ) $\propto I^2$.
- Q (10). Explain the working and construction of attraction type moving iron instrument or voltmeter or ammeter with neat and clean diagram. Mention its merits and demerits.
- Q (11). Write short notes on the following:
a) Deflecting Torque
b) Controlling Torque
c) Damping Torque
- OR
- Q (12). Explain essential torques for indicating instruments.