

SOLUTIONS

Date of issue - 13/9/19

ASSIGNMENT - I

Date of Submission - 13/9/19

1. Refer to class notes.

2. Refer to class notes.

3. given $f = 50 \text{ Hz}$ $I_{\text{rms}} = 20 \text{ A}$

instantaneous equation, $i = I_{\text{max}} \sin(2\pi f t)$

$$i = \sqrt{2} I_{\text{rms}} \sin(2\pi \times 50 \times t) = 20\sqrt{2} \sin(100\pi t) \text{ Ans}$$

a) at $t = 0.0025 \text{ sec}$, $i = ?$ after passing through a positive maximum value.

~~$i = 20\sqrt{2} \sin(100\pi \times 0.0025)$~~
hence instantaneous equation becomes.

$$i = 20\sqrt{2} \sin(100\pi t + \frac{\pi}{2}) = 20\sqrt{2} \cos(100\pi t)$$

$$\therefore i = 20\sqrt{2} \cos(100\pi \times 0.0025) = 20 \text{ A Ans}$$

b) at $t = 0.0125 \text{ sec}$ $i = ?$

$$\therefore i = 20\sqrt{2} \cos(100\pi \times 0.0125) = -20 \text{ A}$$

Now $i = 14.14$, measured from +ve max. value $t = ?$

$$\therefore 14.14 = 20\sqrt{2} \cos(100\pi t)$$

$$t = \frac{1}{100\pi} \cos^{-1}\left(\frac{14.14}{20\sqrt{2}}\right) = \frac{1}{100\pi} \cos^{-1}\left(\frac{1}{2}\right) = \frac{1}{100\pi} \times \frac{\pi}{3} = \frac{1}{300} \text{ Sec or } 3.33 \times 10^{-3} \text{ Sec Ans}$$

4. Since wave form given is non-symmetrical and sinusoidal function.

$\therefore u = 100 \sin \theta$ is the instantaneous equation

$$\text{Avg value, } V_{\text{avg}} = \frac{1}{\pi} \int_0^{\pi} 100 \sin \theta \, d\theta = \frac{100}{\pi} \int_0^{\pi} \sin \theta \, d\theta = \frac{100}{\pi} [-\cos \theta]_0^{\pi}$$

$$V_{\text{avg}} = \frac{100}{\pi} [-\cos \pi + \cos 0] = \frac{100}{\pi} [1 + 1] = \frac{200}{\pi} = 63.66 \text{ volts Ans}$$

$$\text{RMS value, } V_{\text{rms}} = \sqrt{\frac{1}{\pi} \int_0^{\pi} (100 \sin \theta)^2 \, d\theta} = \sqrt{\frac{100^2}{\pi} \int_0^{\pi} \sin^2 \theta \, d\theta}$$

$$\text{using } \cos 2\theta = 1 - 2\sin^2 \theta, \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$V_{\text{rms}} = \sqrt{\frac{100^2}{\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\theta}{2}\right) \, d\theta} = \sqrt{\frac{100^2}{2\pi} \int_0^{\pi} (1 - \cos 2\theta) \, d\theta}$$

$$V_{rms} = \sqrt{\frac{100^2}{2\pi} \left\{ \int_0^\pi 1 d\theta - \int_0^\pi \cos 2\theta d\theta \right\}} = \sqrt{\frac{100^2}{2\pi} \left\{ [\theta]_0^\pi - \left[\frac{\sin 2\theta}{2} \right]_0^\pi \right\}}$$

$$V_{rms} = \sqrt{\frac{100^2}{2\pi} \left\{ (\pi - 0) - \left(\frac{\sin 2\pi}{2} - \frac{\sin 0}{2} \right) \right\}} = \sqrt{\frac{100^2}{2\pi} (\pi)}$$

$$V_{rms} = \frac{100}{\sqrt{2}} = 70.71 \text{ volts } \underline{\underline{\text{Ans}}}$$


$$\text{form factor, } K_f = \frac{V_{rms}}{V_{avg}} = \frac{70.71}{63.66} = 1.11 \underline{\underline{\text{Ans}}}$$

5. given: $V_1 = 100 \sin 500t$, $\phi_1 = 0^\circ$

$V_2 = 200 \sin(500t + \frac{\pi}{3})$, $\phi_2 = \frac{\pi}{3}$

$V_3 = -50 \cos 500t = 50 \sin(500t - \frac{\pi}{2})$, $\phi_3 = -\frac{\pi}{2}$

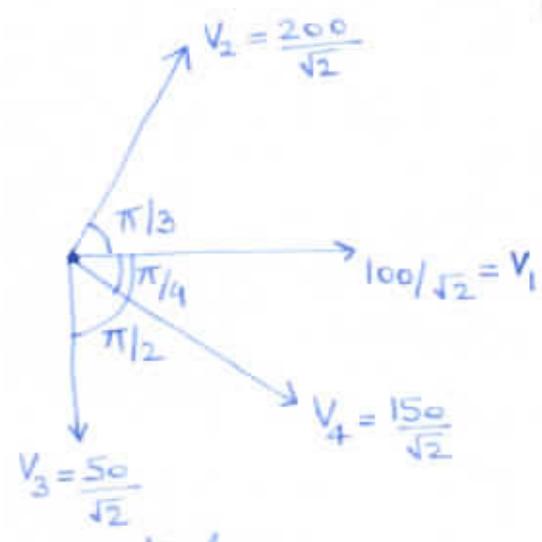$V_4 = 150 \sin(500t - \frac{\pi}{4})$, $\phi_4 = -\pi/4$



phasor diagram

X-component,
 $V_x = 200 \cos 0^\circ + 200 \cos(\pi/3) + 50 \cos(-\pi/2) + 150 \cos(-\pi/4)$
 $V_x = 100 \times 1 + 200 \times 1/2 + 50 \times 0 + 150 \times 1/\sqrt{2} = 306.066 \text{ volts}$

Y-component,
 $V_y = 100 \sin 0^\circ + 200 \sin(\pi/3) + 50 \sin(-\pi/2) + 150 \sin(-\pi/4)$
 $V_y = 100 \times 0 + 200 \times \frac{\sqrt{3}}{2} - 50 \times 1 - 150 \times 1/\sqrt{2} = 17.139 \text{ volts}$


Resultant magnitude, $V_{Rmax} = \sqrt{V_x^2 + V_y^2} = \sqrt{(306.066)^2 + (17.139)^2}$

$V_{Rmax} = 306.545 \text{ volts}$
 $\therefore \text{RMS value, } V_{rms} = \frac{V_{Rmax}}{\sqrt{2}} = \frac{306.545}{\sqrt{2}} = 216.76 \text{ volts } \underline{\underline{\text{Ans}}}$

⑥ given: $i_1 = 10 \sin 314t, \phi_1 = 0^\circ$
 $i_2 = 7.5 \sin(314t - \frac{\pi}{3}), \phi_2 = -\frac{\pi}{3}$
 $i_3 = 12 \sin(314t - \frac{\pi}{4}), \phi_3 = -\frac{\pi}{4}$

X-component, $I_x = 10 \cos 0^\circ + 7.5 \cos(-\frac{\pi}{3}) + 12 \cos(-\frac{\pi}{4})$
 $= 10 \times 1 + 7.5 \times \frac{1}{2} + 12 \times \frac{1}{\sqrt{2}} = 22.235 \text{ amp}$

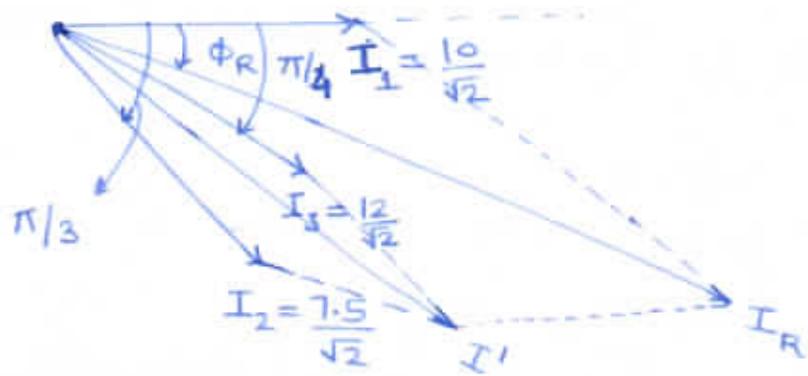Y-component, $I_y = 10 \sin 0^\circ + 7.5 \sin(-\frac{\pi}{3}) + 12 \sin(-\frac{\pi}{4})$
 $= 10 \times 0 + (-7.5 \times \frac{\sqrt{3}}{2}) - 12 \times \frac{1}{\sqrt{2}} = -14.98 \text{ amp}$



phasor diagram

Resultant magnitude, $I_{Rmax} = \sqrt{I_x^2 + I_y^2} = \sqrt{(22.23)^2 + (-14.98)^2}$
 $I_{Rmax} = 26.80 \text{ amp}$


Resultant phase angle $\phi_R = \tan^{-1}(\frac{V_y}{V_x}) = \tan^{-1}(\frac{-14.98}{22.23}) = -0.592 \text{ rad}$

instantaneous equation of resultant current, $i = 26.80 \sin(314t - 0.592)$ Ans


rms value of resultant current, $I_{rms} = \frac{I_{Rmax}}{\sqrt{2}} = \frac{26.80}{\sqrt{2}} = 18.95 \text{ Amp}$ Ans

⑦ please refer class notes. Topic Purely Inductive and purely capacitive circuit of unit-2.

⑧ soln:

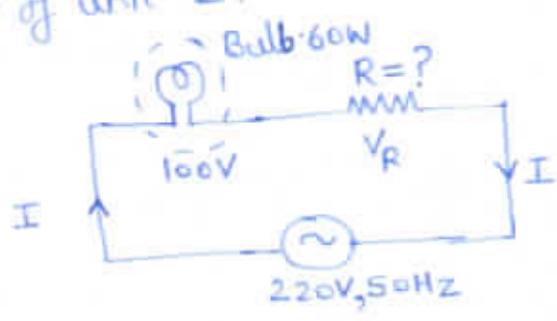

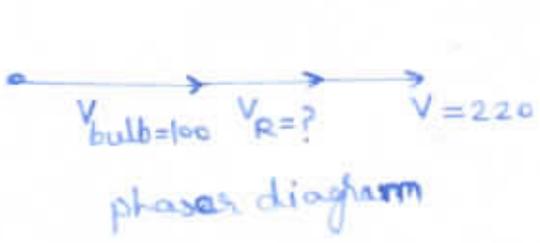current taken by bulb, $I = \frac{60}{100} = \frac{P}{V}$
 $I = 0.6 \text{ A}$
 voltage across unknown resistance 'R'
 $V_R = V - V_{bulb} = 220 - 100 = 120 \text{ V}$
 (because bulb is considered purely resistive)




Unknown resistance, $R = \frac{V_R}{I} = \frac{120}{0.6}$
 $R = 200 \Omega$ Ans

9) Solⁿ: $v = 50 \sin(314t + 55^\circ)$, $\phi_1 = 55^\circ$
 $i = 10 \sin(314t + 325^\circ)$, $\phi_2 = 325^\circ$

phase difference between voltage and current $\phi = \phi_1 - \phi_2$
 $\phi = 55 - 325 = -270^\circ$

\therefore Power drawn $P = VI \cos \phi = \frac{50}{\sqrt{2}} \times \frac{10}{\sqrt{2}} \cos(270^\circ) = 0$ Ans

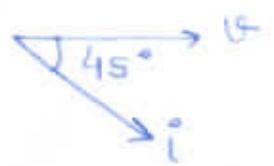10) Solⁿ: given $v = 283 \sin 314t$, $\phi_1 = 0^\circ$
 $i = 4 \sin(314t - 45^\circ)$, $\phi_2 = -45^\circ$



$\therefore \omega = 314$, $f = \frac{314}{2\pi} = 50 \text{ Hz}$
 phase angle,
 $\phi = \phi_1 - \phi_2 = 0 - (-45) = 45^\circ$


power factor, $\cos \phi = \cos(45) = \frac{1}{\sqrt{2}} = 0.707$ lagging ($\because \phi$ is +ve)
 or current is lagging

Resistance $R = Z \cos \phi = \frac{V_{\max}}{I_{\max}} \cos \phi = \frac{283}{4} \times 0.707$
 $R = 50.02 \Omega$ Ans

Inductive reactance, $X_L = Z \sin \phi = \frac{283}{4} \sin(45^\circ) = 50.02 \Omega$

$\therefore X_L = 2\pi f L \Rightarrow L = \frac{X_L}{2\pi f} = \frac{X_L}{\omega} = \frac{50.02}{314} = 0.159 \text{ H}$ Ans

11) Solⁿ:

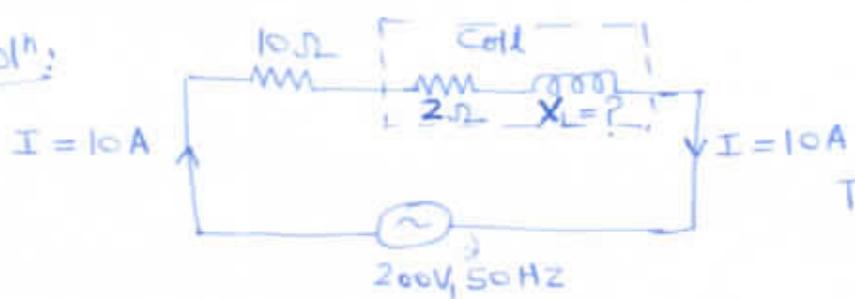

$Z = \frac{V}{I} = \frac{200}{10} = 20 \Omega$
 Total resistance = $10 + 2 = 12 \Omega$

Impedance of the circuit, $Z = \sqrt{(10+2)^2 + X_L^2} = \sqrt{(12)^2 + X_L^2}$

$20 = \sqrt{(12)^2 + X_L^2} \Rightarrow X_L = \sqrt{(20)^2 - (12)^2} = 16 \Omega$

i) Inductance of coil,
 $\therefore L = \frac{X_L}{2\pi f} = \frac{16}{2\pi \times 50} = 0.0509 \text{ H}$ Ans

Impedance of coil, $Z_{\text{coil}} = \sqrt{R_{\text{coil}}^2 + X_L^2} = \sqrt{(2)^2 + (16)^2} = 16.124 \Omega$

ii) power factor of coil, $\cos \phi_{\text{coil}} = \frac{R_{\text{coil}}}{Z_{\text{coil}}} = \frac{2}{16.124} = 0.1240$ (lagging) Ans


power factor of circuit, $\cos \phi = \frac{R_{\text{Total}}}{Z} = \frac{12}{20} = 0.6$ lagging Ans

iii) quality factor of coil, Q-factor = $\frac{\omega L}{R_{\text{coil}}} = \frac{X_L}{R_{\text{coil}}} = \frac{16}{2} = 8$ Ans

iv) voltage across coil, $V_{\text{coil}} = I Z_{\text{coil}} = 10 \times 16.124 = 161.24$ volts Ans

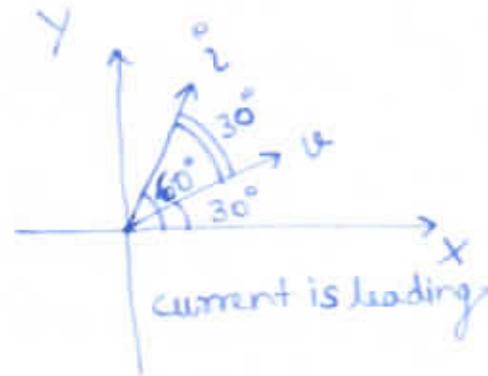(13) given: $v = 100 \sin(\omega t + 30^\circ)$ $\phi_1 = 30^\circ$
 $i = 20 \sin(\omega t + 60^\circ)$ $\phi_2 = 60^\circ$

phase angle, $\phi = \phi_1 - \phi_2 = 30 - 60 = -30^\circ$
 since ϕ is "ve" hence current is leading.



impedance, $Z = \frac{V_{\text{max}}}{I_{\text{max}}} = \frac{100}{20} = 5 \Omega$ Ans

resistance $R = Z \cos \phi = 5 \cos(30) = 5 \times \frac{\sqrt{3}}{2} = 4.33 \Omega$ Ans

reactance $X = Z \sin \phi = 5 \sin(30) = 5 \times \frac{1}{2} = 2.5 \Omega$ (capacitive) Ans
 (\because current is leading)

power factor, $\cos \phi = \cos(30^\circ) = \frac{\sqrt{3}}{2} = 0.866$ (leading) Ans

power, $P = V I \cos \phi = \frac{100}{\sqrt{2}} \times \frac{20}{\sqrt{2}} \times 0.866 = 866$ watts Ans

(14) given: $R = 10 \Omega$, $L = 0.1 \text{ H}$, $C = 50 \mu\text{F}$, $v(t) = 141.4 \cos(100\pi t)$.

from voltage equation, $\omega = 100\pi$ rad/sec.

Now, ii) $X_L = \omega L = 100\pi \times 0.1 = 31.415 \Omega$ Ans

iii) $X_C = \frac{1}{\omega C} = \frac{1}{100\pi \times 50 \times 10^{-6}} = 63.661 \Omega$ Ans

Impedance of the circuit, $Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(10)^2 + (31.415 - 63.661)^2}$
 $Z = 33.76 \Omega$

phase angle of the circuit, $\phi = \tan^{-1}\left(\frac{X_C - X_L}{R}\right)$
 $\phi = \tan^{-1}\left(\frac{63.661 - 31.415}{10}\right) = 72.77^\circ$

\therefore expression for instantaneous current,
 $i = \frac{V_{max}}{Z} \cos(100\pi t + 72.77^\circ) = \frac{141.4}{33.76} \cos(100\pi t + 72.77^\circ)$

i) $i = 4.188 \cos(100\pi t + 72.77^\circ)$ amp Ans

ii) power factor of circuit, $\cos\phi = \cos(72.77^\circ) = 0.2962$ (leading) Ans
 (because $X_C > X_L$)

iv) voltage drop across resistance, $V_R = IR = \frac{4.188}{\sqrt{2}} \times 10 = 29.61$ volts Ans

voltage drop across inductance, $V_L = IX_L = \frac{4.188}{\sqrt{2}} \times 31.415 = 93.03$ volts Ans


voltage drop across capacitor, $V_C = IX_C = \frac{4.188}{\sqrt{2}} \times 63.661 = 188.52$ volts Ans

v) Active Power = $VI \cos\phi = \frac{141.4}{\sqrt{2}} \times \frac{4.188}{\sqrt{2}} \times 0.2962 = 87.702$ watts Ans

Reactive power = $VI \sin\phi = \frac{141.4}{\sqrt{2}} \times \frac{4.188}{\sqrt{2}} \times \sin(72.77^\circ)$
 $= 282.804$ VAR Ans

Apparent power, $= VI = \frac{141.4}{\sqrt{2}} \times \frac{4.188}{\sqrt{2}} = 296.091$ VA Ans

12) given:

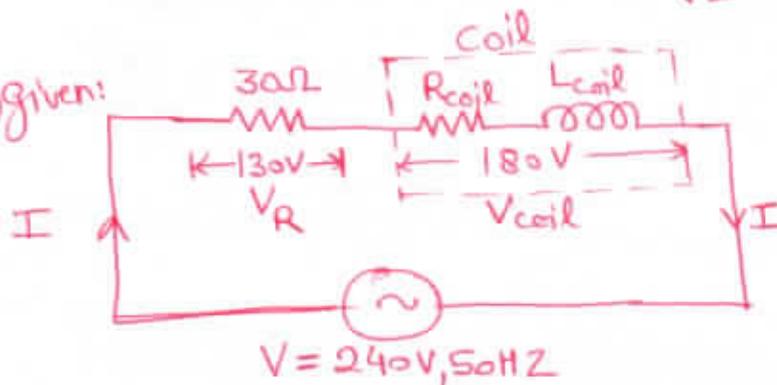

current in circuit,


$I = \frac{130}{30} = 4.33$ A

from phasor diagram,

$OC^2 = OB^2 + BC^2$

$OC^2 = (OA + AB)^2 + BC^2$

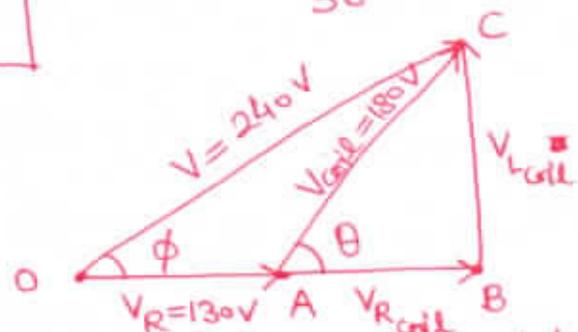$(240)^2 = (130 + 180 \cos\theta)^2 + (180 \sin\theta)^2$



phasor diagram of the ckt

(16) given: $v = 100 \sin(314t - \pi/4)$ volts


$i = 20 \sin(314t - 90^\circ) = 20 \sin(314t - \pi/2)$ amps.

hence $\omega = 314$ rad/sec

since phase angle $\phi = -\frac{\pi}{4} - (-\frac{\pi}{2})$

$$\phi = -\frac{\pi}{4} + \frac{\pi}{2} = \frac{-2\pi + \pi}{4}$$

$$\phi = \pi/4 = 45^\circ$$

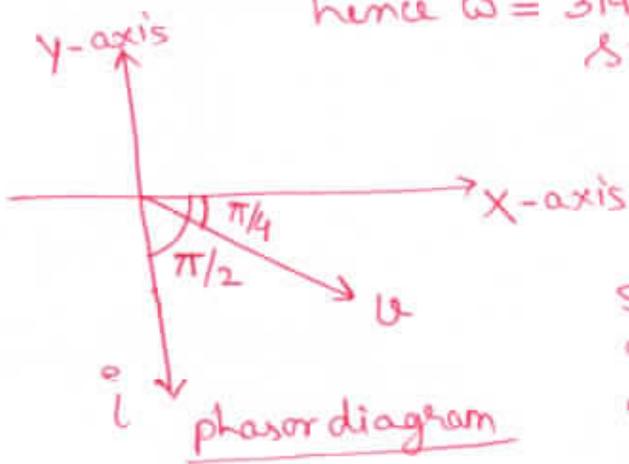

since phase angle is 45° and is positive and also phase diagram shows that current is lagging behind voltage by $\pi/4$ rad. Hence circuit has two elements namely resistance and inductance.

$$\therefore Z = \frac{V_{max}}{I_{max}} = \frac{100}{20} = 5 \Omega$$

$$\therefore R = Z \cos \phi = 5 \cos(45) = 5 \times 1/\sqrt{2} = 3.53 \Omega \text{ Ans}$$

$$\& X_L = Z \sin \phi = 5 \sin(45) = 3.53 \Omega$$

$$\therefore X_L = 2\pi fL, L = \frac{X_L}{2\pi f} = \frac{X_L}{\omega} = \frac{3.53}{314} = \del{0.0112} 0.0112 \text{ H}$$

$$\text{or } L = \del{1.2} 1.2 \text{ mH Ans}$$

$$\text{since } \omega = 2\pi f = 314$$

$$\therefore f = \frac{\omega}{2\pi} = \frac{314}{2\pi} = 50 \text{ Hz Ans}$$

(17) given: $R_{coil} = 8 \Omega$, $L_{coil} = 0.12 \text{ H}$, $C = 140 \mu\text{F} = 140 \times 10^{-6} \text{ F}$
 $V = 230 \text{ volts}$, $f = 50 \text{ Hz}$.

$$X_L = 2\pi f L_{coil} = 2\pi \times 50 \times 0.12 = 37.69 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 140 \times 10^{-6}} = 22.73 \Omega$$

$$i) Z = \sqrt{R_{coil}^2 + (X_L - X_C)^2} = \sqrt{(8)^2 + (37.69 - 22.73)^2} = 16.96 \Omega \text{ Ans}$$

$$ii) I_{condenser} = \frac{V}{Z} = \frac{230}{16.96} = 13.55 \text{ Amp Ans}$$

$$iii) \cos \phi = \frac{R_{coil}}{Z} = \frac{8}{16.96} = 0.4716 \text{ lagging } (\because X_L > X_C) \text{ Ans}$$

(7)

$$(240)^2 = (130)^2 + (180)^2 \cos^2 \theta + 2 \times 130 \times 180 \cos \theta + (180)^2 \sin^2 \theta$$

$$(240)^2 = (130)^2 + (180)^2 [\cos^2 \theta + \sin^2 \theta] + 2 \times 130 \times 180 \cos \theta$$

$$(240)^2 = (130)^2 + (180)^2 + 46800 \cos \theta$$

$$46800 \cos \theta = (240)^2 - \{(130)^2 + (180)^2\}$$

$$46800 \cos \theta = 8300$$

$$\cos \theta = \frac{83}{468} = 0.17735$$

$$\text{or } \theta = \cos^{-1}(0.177) = 79.78^\circ$$

$$\therefore V_{R_{\text{coil}}} = 180 \cos \theta = 180 \times 0.177 = 31.92 \text{ volts}$$

$$\therefore R_{\text{coil}} = \frac{V_{R_{\text{coil}}}}{I} = \frac{31.92}{4.33} = 7.37 \Omega$$

i) power consumed by the coil, $P_{\text{coil}} = V_{\text{coil}} I_{\text{coil}} \cos \phi_{\text{coil}}$
 or $P_{\text{coil}} = I^2 R_{\text{coil}} = (4.33)^2 \times 7.37 = 138.22 \text{ watts}$ Ans

ii) Power factor of the whole circuit,

$$\cos \phi = \frac{R_T}{Z} = \frac{30 + 7.37}{55.43} = 0.6741 \text{ Ans } \quad \therefore Z = \frac{V}{I} = \frac{240}{4.33} = 55.43 \Omega$$

lagging

(15) given: $L = 50 \text{ mH} = 50 \times 10^{-3} \text{ H}$; $Z = 20 \Omega$; $\cos \phi = 0.5$ lagging.

as we know that, $R = Z \cos \phi = 20 \times 0.5 = 10 \Omega$

\therefore Resistance of coil $R = 10 \Omega$ Ans $\therefore \cos \phi = 0.5$ $\sin \phi = \sqrt{1 - (0.5)^2}$
 $\phi = 60^\circ$ $\sin \phi = \sqrt{3}/2$

since $X_L = Z \sin \phi = 20 \times \sin 60^\circ = 20 \times \sqrt{3}/2$


$$X_L = 17.32 \Omega$$

as we know that, $X_L = \omega L$

$$\therefore \omega = \frac{X_L}{L} = \frac{17.32}{50 \times 10^{-3}} = 346.41 \text{ rad/sec}$$
 Ans

iv) voltage across capacitor, $V_c = I X_c = 13.55 \times 22.73$
 $V_c = 307.99$ volts. Ans

(9)

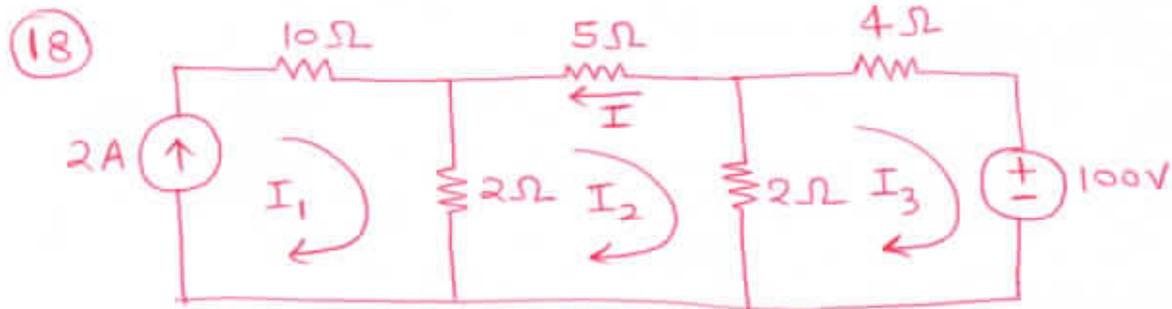

Since $I_1 = 2$ since $I_1 = 2A$ (given)

KVL equation of mesh II

$$-2(I_2 - 2) - 5I_2 - 2(I_2 - I_3) = 0$$

$$0I_1 - 9I_2 + 2I_3 = -4 \quad \text{--- (I)}$$

KVL equation of mesh III


$$-2(I_3 - I_2) - 4I_3 - 100 = 0$$

$$2I_2 - 6I_3 = 100 \quad \text{--- (II)}$$

Solving eq. (I) & eq. (II) we get,

$$I_2 = -3.52A \quad I_3 = -17.84A$$

$$I = -I_2 = 3.52A \quad \text{Ans}$$

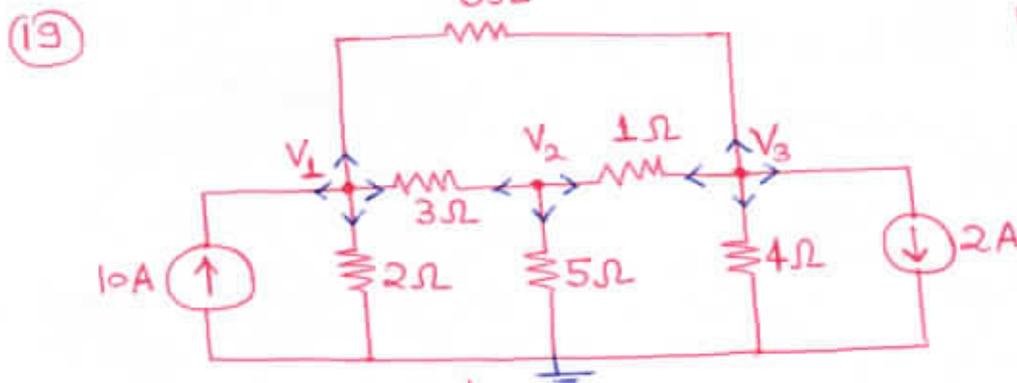

applying KCL at node-1

$$-10 + \frac{V_1}{2} + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{5} = 0$$

$$-300 + 15V_1 + 10V_1 - 10V_2 + 6V_1 - 6V_3 = 0$$

$$31V_1 - 10V_2 - 6V_3 = 300 \quad \text{--- (1)}$$

applying KCL at node-2

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - V_3}{1} = 0$$

$$\frac{5V_2 - 5V_1 + 3V_2 + 15V_2 - 15V_3}{15} = 0$$

$$-5V_1 + 23V_2 - 15V_3 = 0 \quad \text{--- (2)}$$

applying KCL at node-3

$$\frac{V_3 - V_1}{5} + \frac{V_3 - V_2}{1} + \frac{V_3}{4} + 2 = 0$$

$$\frac{4V_3 - 4V_1 + 20V_3 - 20V_2 + 5V_3 + 40}{20} = 0$$

$$-4V_1 - 20V_2 + 29V_3 = -40 \quad \text{--- (3)}$$

solving eq. ①, ② & ③ we get,

$V_1 = 12.06 \text{ volts}$; $V_2 = 5.1 \text{ volts}$; $V_3 = 3.8 \text{ volts}$
or 5.1009

Now from circuit diagram:

$I_1 = \frac{V_1 - V_3}{5} = \frac{12.06 - 3.8}{5} = 1.652 \text{ A}$ Ans


$I_2 = \frac{V_1 - V_2}{3} = \frac{12.06 - 5.1}{3} = 2.32 \text{ A}$ Ans

$I_3 = \frac{V_1}{2} = \frac{12.06}{2} = 6.03 \text{ A}$ Ans

$I_4 = \frac{V_2}{5} = \frac{5.1}{5} = 1.02 \text{ A}$ Ans

$I_5 = \frac{V_3}{4} = \frac{3.8}{4} = 0.95 \text{ A}$ Ans

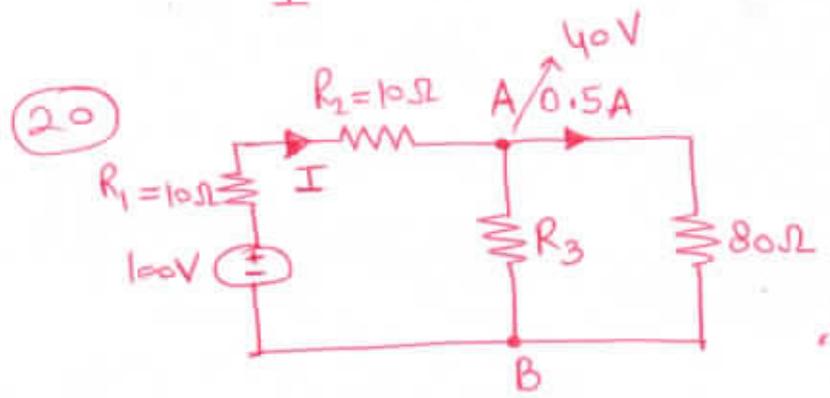
$I_6 = \frac{V_2 - V_3}{1} = 5.1 - 3.8 = 1.3 \text{ A}$ Ans



voltage at node A = $0.5 \times 80 = 40 \text{ V}$

\therefore current $I = \frac{100 - 40}{10 + 10} = 3 \text{ A}$

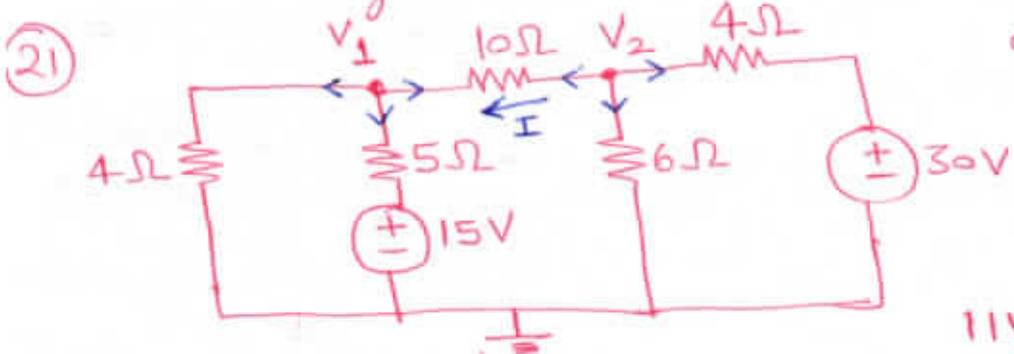\therefore voltage drop across $R_1 = 3 \times 10 = 30 \text{ volts}$
 voltage drop across $R_2 = 3 \times 10 = 30 \text{ volts}$ } Ans



applying KCL at node-1

$\frac{V_1}{4} + \frac{V_1 - 15}{5} + \frac{V_1 - V_2}{10} = 0$

$\frac{5V_1 + 4V_1 - 60 + 2V_1 - 2V_2}{20} = 0$

$11V_1 - 2V_2 = 60$ — (1)

applying KCL at node-2

$\frac{V_2 - V_1}{10} + \frac{V_2}{6} + \frac{V_2 - 30}{4} = 0 \Rightarrow \frac{6V_2 - 6V_1 + 10V_2 + 15V_2 - 450}{60} = 0$

$$6V_2 - 6V_1 + 10V_2 + 15V_2 = 450$$


$$-6V_1 + 31V_2 = 450 \text{ --- (2)}$$

Solving eq. (1) & eq. (2) we get,

$$V_1 = 8.389 \text{ volts ; } V_2 = 16.139 \text{ volts}$$

$$\text{hence } I = \frac{V_2 - V_1}{10} = \frac{16.139 - 8.389}{10} = 0.7750 \text{ A } \underline{\underline{\text{Ans}}}$$

(22) Considering 6V source.

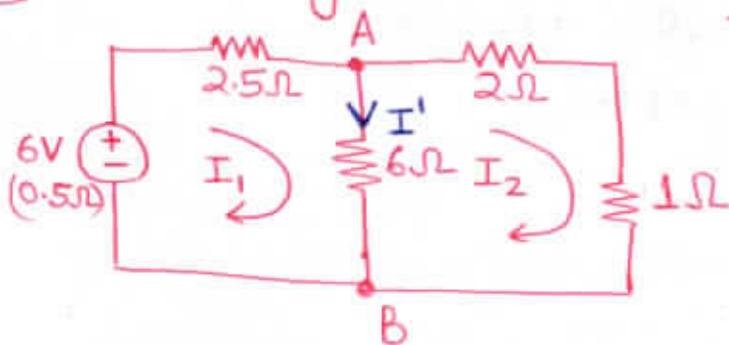

KVL equation of mesh-1

$$-0.5I_1 + 6 - 2.5I_1 - 6(I_1 - I_2) = 0$$

$$-9I_1 + 6I_2 = -6 \text{ --- (1)}$$

KVL equation of mesh-2

$$-6(I_2 - I_1) - 2I_2 - 1I_2 = 0$$


$$6I_1 - 9I_2 = 0 \text{ --- (2)}$$

Solving eq. (1) & (2) we get,

$$I_1 = 1.2 \text{ A , } I_2 = 0.8 \text{ A}$$

$$\therefore I' = I_1 - I_2 = 1.2 - 0.8 = 0.4 \text{ A } (\downarrow)$$

Considering 12V source :

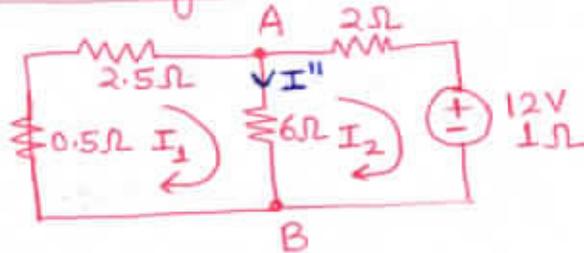

KVL equation of mesh-1

$$-0.5I_1 - 2.5I_1 - 6(I_1 - I_2) = 0$$

$$-9I_1 + 6I_2 = 0 \text{ --- (3)}$$

KVL equation of mesh-2

$$-6(I_2 - I_1) - 2I_2 - 12 - 1I_2 = 0$$

$$6I_1 - 9I_2 = 12 \text{ --- (4)}$$


Solving eq. (3) and (4) we get,

$$I_1 = -1.6 \text{ A ; } I_2 = -2.4 \text{ A ;}$$

$$\therefore I'' = I_1 - I_2 = -1.6 - (-2.4) = 0.8 \text{ A } (\downarrow)$$

Hence current in branch AB, $I = I' + I'' = 0.4 \text{ A} + 0.8 \text{ A} = 1.2 \text{ A } (\downarrow) \underline{\underline{\text{Ans}}}$

23 Consider 90V source:

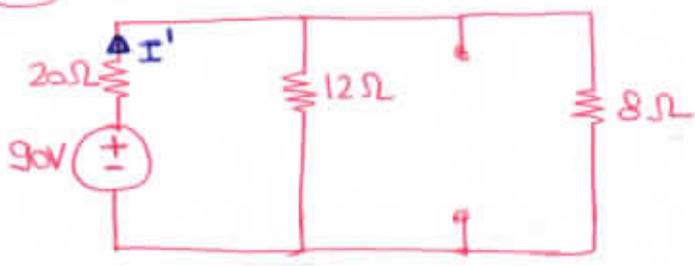


$$R_{eq} = (12 || 8) + 20 = \left(\frac{12 \times 8}{12+8}\right) + 20$$

$$R_{eq} = 24.8 \Omega$$

$$\therefore I' = \frac{90}{24.8} = 3.629 \text{ A } (\uparrow)$$

Consider 60V source

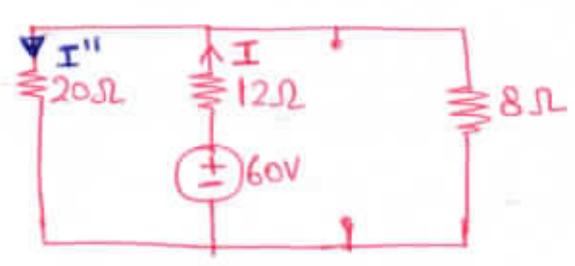

Req for 60V source,



$$R_{eq} = (20 || 8) + 12 = \frac{20 \times 8}{20+8} + 12$$

$$R_{eq} = 17.71 \Omega$$

$$I = \frac{60}{17.71} = 3.38 \text{ A}$$

$$\therefore I'' = I \times \frac{8}{20+8} = 3.38 \times \frac{8}{28} = 0.967 \text{ A } (\downarrow)$$

Consider 2A source

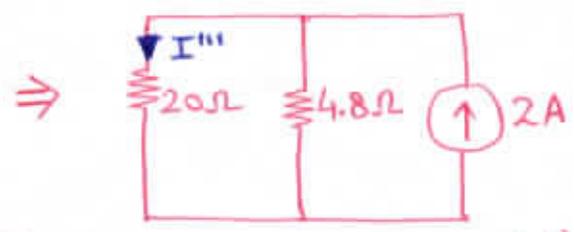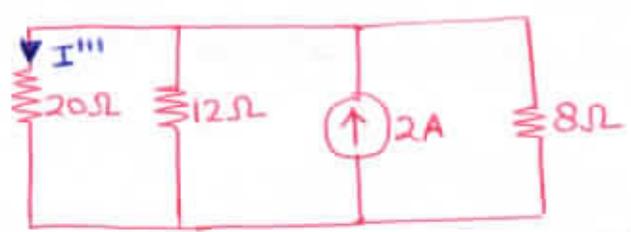


$$\left(\frac{12 || 8}{12+8}\right) = 4.8 \Omega$$

$$I''' = 2 \times \frac{4.8}{20+4.8} = 0.387 \text{ A } (\downarrow)$$

Hence current in 20Ω resistor = $I' - (I'' + I''') = 3.629 - (0.967 + 0.387)$
 $= 3.629 - (0.967 + 0.387) = 2.275 \text{ A } (\uparrow)$ Ans

24 Circuit diagram for V_{TH};

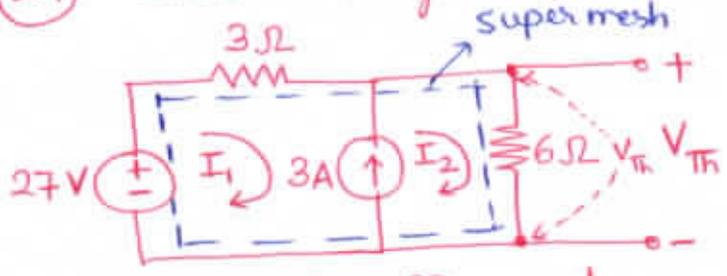

First equation; $I_2 - I_1 = 3$
 $\Rightarrow -I_1 + I_2 = 3$ — (1)


Equation of supermesh,
 $27 - 3I_1 - 6I_2 = 0$
 $3I_1 + 6I_2 = 27$ — (2)

Solving eq. (1) & eq. (2) we get,

$$I_1 = 1 \text{ A}, I_2 = 4 \text{ A}$$


\therefore voltage across 6Ω resistor i.e. $V_{TH} = 6I_2 = 6 \times 4 = 24 \text{ volts}$.

Circuit diagram of R_{Th}

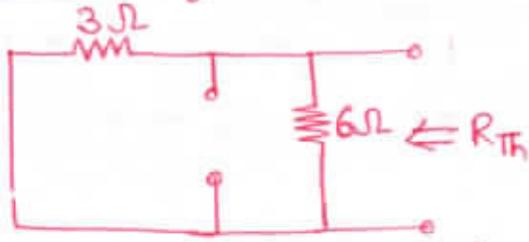


$$R_{Th} = (3 || 6) = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \Omega$$

Thevenin's Equivalent circuit:

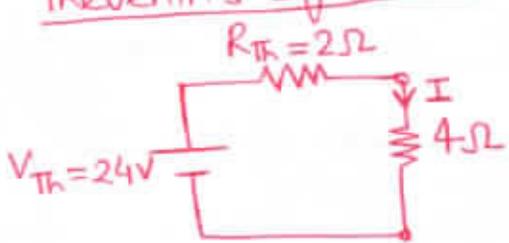

$$\therefore I = \frac{24}{2+4} = 4 \text{ A } \underline{\underline{\text{Ans}}}$$

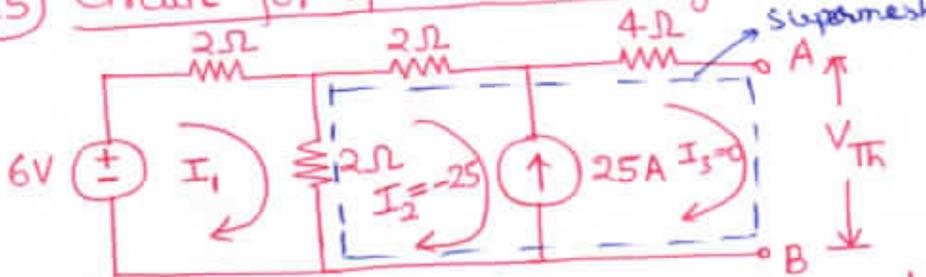(25) Circuit for open circuit voltage i.e V_{Th} :



First equation from super mesh,
 $I_3 - I_2 = 25$
 $0 - I_2 = 25, I_2 = -25 \text{ A}$

KVL equation for mesh-I

$$6 - 2I_1 - 2[I_1 - (-25)] = 0$$

$$6 - 2I_1 - 2I_1 - 50 = 0$$

$$-4I_1 - 44 = 0$$

$$I_1 = -11 \text{ A}$$


Equation of supermesh;

$$-2(-25 - I_1) - 2(-25) - 4(0) - V_{Th} = 0$$

$$50 + 2(-11) + 50 - V_{Th} = 0$$

$$V_{Th} = 78 \text{ volts } \underline{\underline{\text{Ans}}}$$

Circuit for R_{Th}

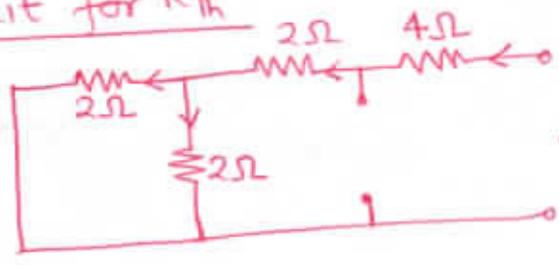


$$R_{Th} = \left\{ (2 || 2) \right\} + (2+4)$$

$$\leftarrow R_{Th} = \left\{ \frac{2 \times 2}{2+2} \right\} + 6$$


$$R_{Th} = 7 \Omega \underline{\underline{\text{Ans}}}$$

Thevenin's Equivalent circuit;

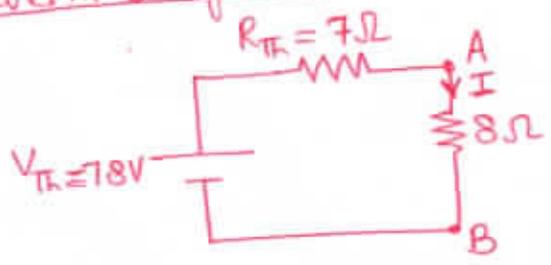

$$I = \frac{78}{7+8} = 5.2 \text{ A } \underline{\underline{\text{Ans}}}$$

26) Circuit for I_N ;

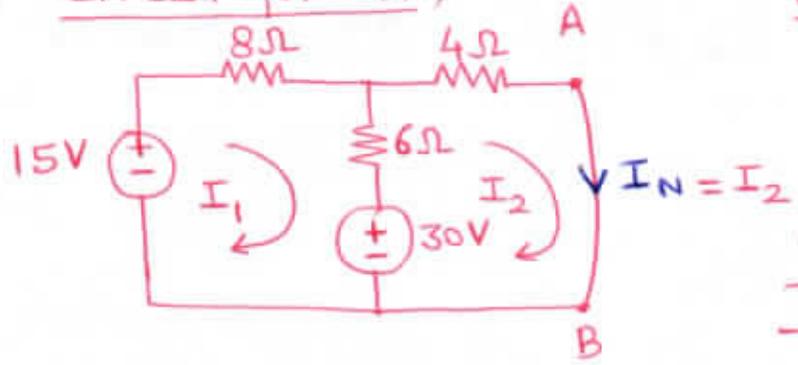

KVL equation of mesh-1

$$15 - 8I_1 - 6(I_1 - I_2) - 30 = 0$$

$$-14I_1 + 6I_2 = 15 \quad \text{--- (1)}$$


KVL equation of mesh-2

$$-6(I_2 - I_1) - 4I_2 + 30 = 0$$

$$6I_1 - 10I_2 = -30 \quad \text{--- (2)}$$

Solving eq. (1) & (2) we get,
 $I_1 = 0.288 \text{ A}$, $I_2 = 3.173 \text{ A}$ Hence $I_N = 3.173 \text{ A}$


Circuit for R_N ;

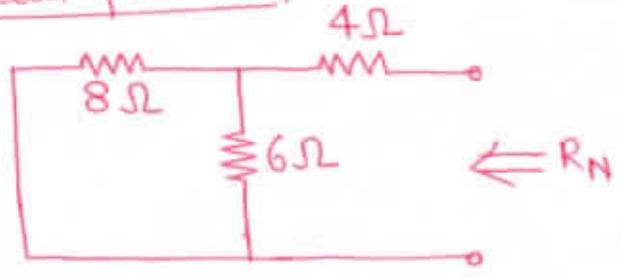

$$R_N = (8 \parallel 6) + 4 = \left(\frac{8 \times 6}{8 + 6}\right) + 4$$

$$R_N = 7.428 \Omega$$

Norton's Equivalent Circuit;

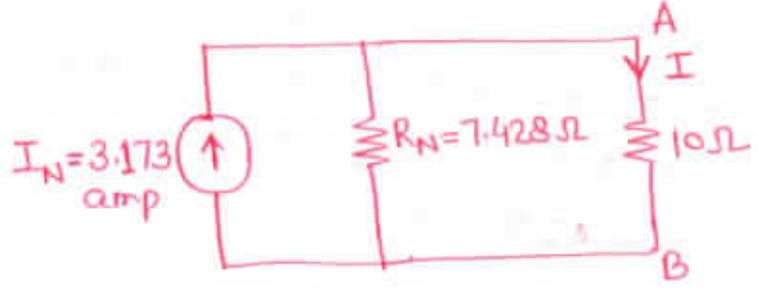


~~I_N~~ : $I = I_N \times \frac{R_N}{R_N + R_L}$

$$I = 3.173 \times \frac{7.428}{7.428 + 10}$$

$$I = 1.352 \text{ A} \quad \underline{\underline{\text{Ans}}}$$


27) Circuit for I_N ;

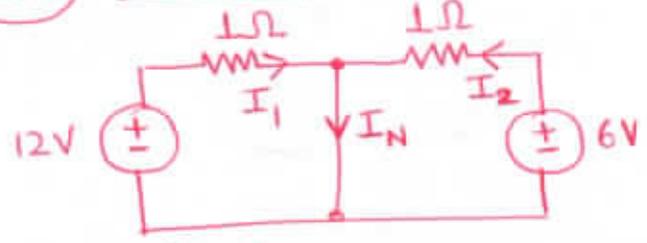

In fig (9): $I_N = I_1 + I_2$


$$I_N = \frac{12}{1} + \frac{6}{1} = 18 \text{ A}$$

Circuit for R_N

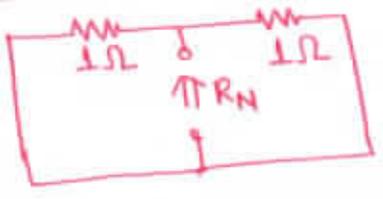

$$R_N = 1 \parallel 1 = \frac{1}{2} = 0.5 \Omega$$


Norton's Equivalent Circuit;

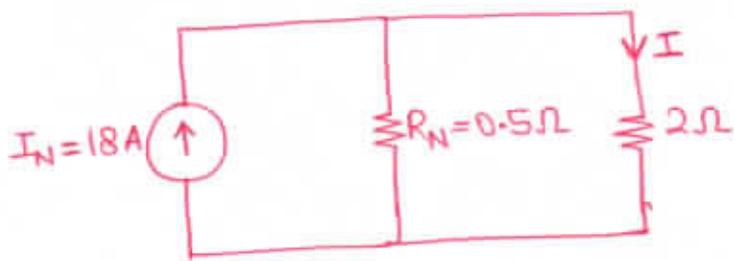

$$\therefore I = 18 \times \frac{0.5}{0.5+2}$$

$$I = 3.6 \text{ A Ans}$$

Q28.



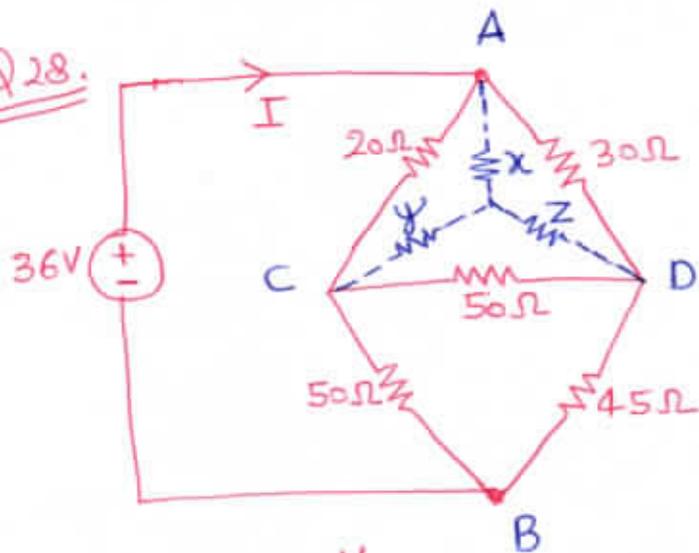


using delta to star conversion in network ADC,

$$x = \frac{20 \times 30}{20+30+50} = 6\Omega$$

$$y = \frac{20 \times 50}{20+30+50} = 10\Omega$$
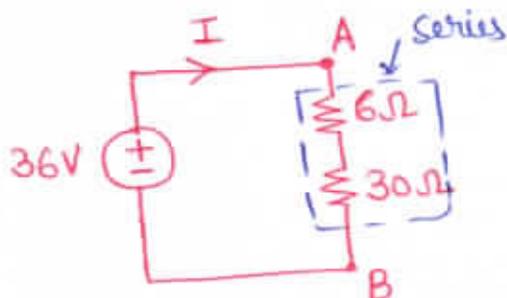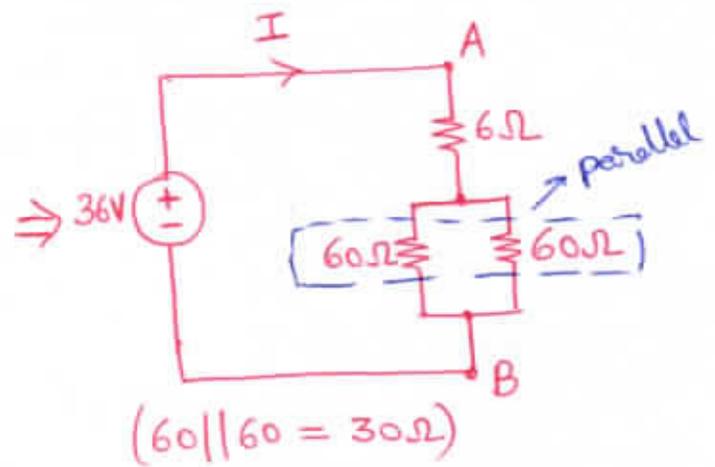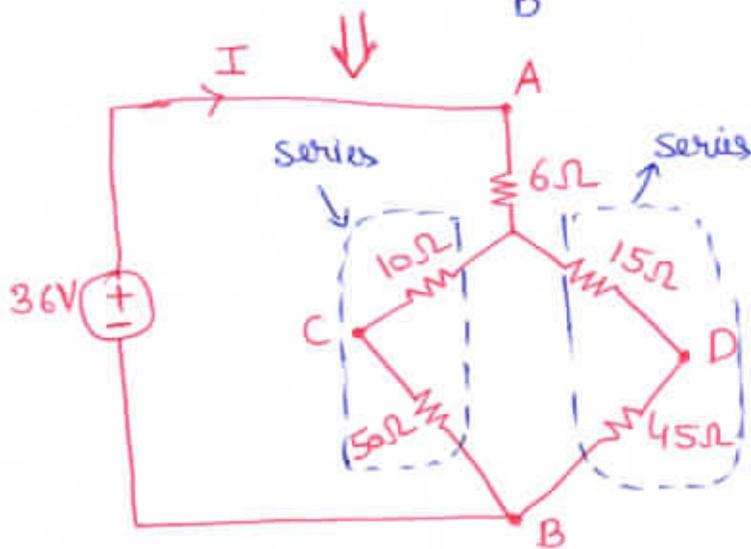
$$z = \frac{30 \times 50}{20+30+50} = 15\Omega$$



$$\Rightarrow I = \frac{36}{36} = 1 \text{ A Ans}$$

