

Date of Exam: 3/10/19

Ans 1 a): Q-factor = $\tan \phi = \tan 45^\circ = 1$ Ans

Ans 1 b): $Z = 6 + j8$; $Y = \frac{6}{6^2+8^2} - j \frac{8}{6^2+8^2} = (0.06 - j 0.08) \Omega^{-1}$

\therefore conductance = $0.06 \Omega^{-1}$ and susceptance = $0.08 \Omega^{-1}$ Ans


Ans 1 c): given: $v = 100 \sin(314t + 55^\circ)$ volts ; $i = 15 \sin(314t + 325^\circ)$ Amp,

$\phi = 55 - 325 = -270^\circ$

\therefore Power = $\frac{V_{\max}}{\sqrt{2}} \times \frac{I_{\max}}{\sqrt{2}} \cos \phi = \frac{100}{\sqrt{2}} \times \frac{15}{\sqrt{2}} \cos(270) = 0$ Ans

Ans 1 d): power factor = 1 Ans

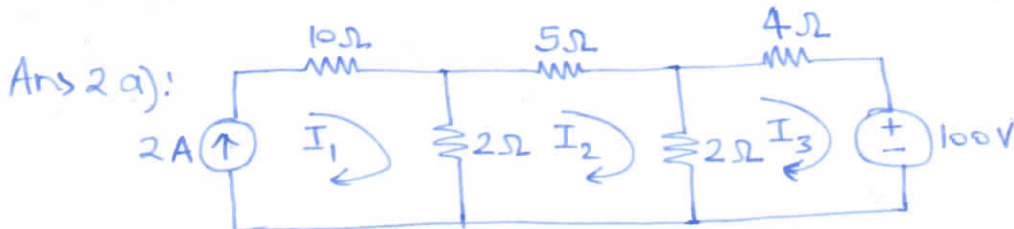Ans 1 e): Internal resistance of ideal voltage source = 0 (zero)
Internal resistance of ideal current source = ∞ (infinite)



$I_1 = 2 \text{ A}$


KVL equation of mesh II: $-2(I_2 - 2) - 5I_2 - 2(I_2 - I_3) = 0$
 $-9I_2 + 2I_3 = -4$ — (I)

KVL equation of mesh III: $-2(I_3 - I_2) - 4I_3 - 100 = 0$
 $2I_2 - 6I_3 = 100$ — (II)

Solving eq. (I) & (II) we get, $I_2 = -3.52 \text{ A}$ $I_3 = -17.84 \text{ A}$

$\therefore I = -I_2 = 3.52 \text{ A}$ Ans

Ans 2 b):

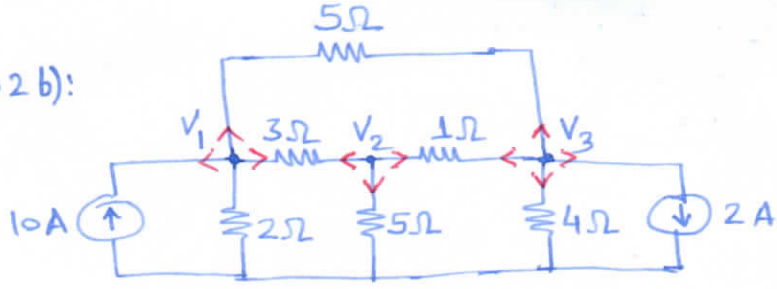

applying KCL at node-1

$$-10 + \frac{V_1}{2} + \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{5} = 0$$

$$-300 + 15V_1 + 10V_1 - 10V_2 + 6V_1 - 6V_3 = 0$$

$$31V_1 - 10V_2 - 6V_3 = 300 \quad \text{--- (1)}$$

applying KCL at node-2

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - V_3}{1} = 0$$

$$5V_2 - 5V_1 + 3V_2 + 15V_2 - 15V_3 = 0$$

$$-5V_1 + 23V_2 - 15V_3 = 0 \quad \text{--- (2)}$$

applying KCL at node-3

$$\frac{V_3 - V_1}{5} + \frac{V_3 - V_2}{1} + \frac{V_3}{4} + 2 = 0$$

$$4V_3 + 4V_1 + 20V_3 - 20V_2 + 5V_3 + 40 = 0$$

$$-4V_1 - 20V_2 + 29V_3 = -40 \quad \text{--- (3)}$$

solving eq. (1), (2) & (3) we get,

$$V_1 = 12.06 \text{ volts}; V_2 = 5.1 \text{ volts}$$

$$V_3 = 3.8 \text{ volts}$$

$$I_1 = \frac{V_1 - V_3}{5} = \frac{12.06 - 3.8}{5} = 1.652 \text{ A}$$

$$I_2 = \frac{V_1 - V_2}{3} = \frac{12.06 - 5.1}{3} = 2.32 \text{ A}$$

$$I_3 = \frac{V_1}{2} = \frac{12.06}{2} = 6.03 \text{ A}; I_4 = \frac{V_2}{4} = \frac{5.1}{5} = 1.02 \text{ A}; I_5 = \frac{V_3}{4} = \frac{3.8}{4} = 0.95 \text{ A}$$

$$I_6 = \frac{V_2 - V_3}{1} = 5.1 - 3.8 = 1.3 \text{ A}$$

Ans 2 c): given $v = 100 \sin(\omega t + 30^\circ)$ $\phi_1 = 30^\circ$
 $i = 20 \sin(\omega t + 60^\circ)$ $\phi_2 = 60^\circ$

$\therefore \phi = 30^\circ - 60^\circ = -30^\circ$ since ϕ is -ve current is leading

impedance $Z = \frac{V_{max}}{I_{max}} = \frac{100}{20} = 5 \Omega$ Ans

Resistance $R = Z \cos \phi = 5 \cos(30) = 4.33 \Omega$ Ans

Reactance $X_C = Z \sin \phi = 5 \sin(30) = 2.5 \Omega$ (capacitive because current is leading)

power factor = $\cos \phi = \cos(30) = 0.866$ (leading) Ans

Power = $V I \cos \phi = \frac{100}{\sqrt{2}} \times \frac{20}{\sqrt{2}} \times \cos 30 = 866 \text{ watt}$ Ans

Ans 2 d): In a series resonant circuit, Quality factor is defined as, Q-factor = $\frac{\text{voltage across L or C at resonance}}{\text{voltage of the circuit at resonance}}$.

Consider case of inductor,
Q-factor = $\frac{\text{voltage across 'L' at resonance}}{\text{voltage of the ckt at resonance}} = \frac{V_{L_0}}{V} = \frac{I_{\text{max}} X_{L_0}}{I_{\text{max}} R}$

Q-factor = $\frac{X_{L_0}}{R} = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$ using $f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$

Q-factor = $\frac{2\pi L}{R} \times \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{R} \sqrt{\frac{L^2}{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$

Now consider case of capacitor,
Q-factor = $\frac{\text{voltage across 'C' at resonance}}{\text{voltage of the circuit at resonance}} = \frac{V_{C_0}}{V} = \frac{I_{\text{max}} X_{C_0}}{I_{\text{max}} R}$

Q-factor = $\frac{X_{C_0}}{R} = \frac{1}{\omega_0 CR} = \frac{1}{2\pi f_0 CR} = \frac{1}{2\pi CR} \times \frac{1}{2\pi \sqrt{LC}} = \frac{1}{CR} \sqrt{\frac{LC}{1}}$

Q-factor = $\frac{1}{R} \sqrt{\frac{LC}{C^2}} = \frac{1}{R} \sqrt{\frac{L}{C}}$

Hence expression of quality factor in series resonant ckt = $\frac{1}{R} \sqrt{\frac{L}{C}}$

Ans 3 a): $V_1 = 100 \sin 500t$; $V_2 = 200 \sin(500t + \frac{\pi}{3})$

$V_3 = -50 \cos 500t = 50 \sin(500t - \frac{\pi}{2})$


$V_4 = 150 \sin(500t - \frac{\pi}{4})$

$\phi_1 = 0^\circ$, $\phi_2 = \pi/3$, $\phi_3 = -\pi/2$, $\phi_4 = -\pi/4$

Resolving in horizontal component,

$V_x = 100 \cos 0^\circ + 200 \cos(\pi/3) + 50 \cos(-\pi/2) + 150 \cos(-\pi/4)$

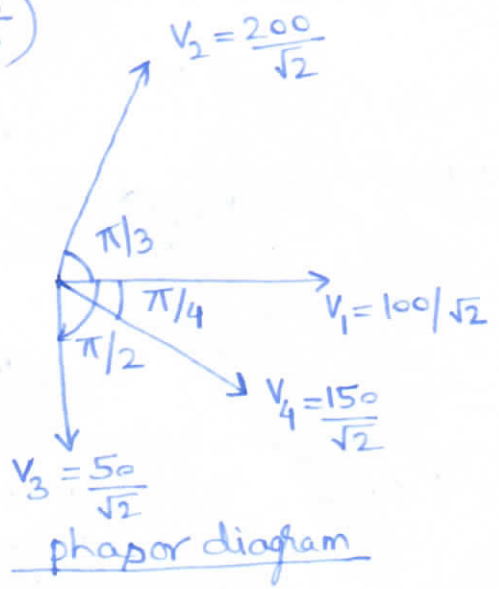$V_x = 100 \times 1 + 200 \times \frac{1}{2} + 50 \times 0 + 150 \times \frac{1}{\sqrt{2}} = 306.066 \text{ volts}$



Resolving verticle component;

$$V_y = 100 \sin 0^\circ + 200 \sin\left(\frac{\pi}{3}\right) + 50 \sin\left(-\frac{\pi}{2}\right) + 150 \sin\left(-\frac{\pi}{4}\right)$$


$$V_y = 100 \times 0 + 200 \times \frac{\sqrt{3}}{2} - 50 \times 1 - 150 \times \frac{1}{\sqrt{2}} = 17.139 \text{ volts}$$

Resultant magnitude; $V_{max R} = \sqrt{V_x^2 + V_y^2} = \sqrt{(306.066)^2 + (17.139)^2}$

$$V_{max R} = 306.545$$

\therefore Resultant rms value, $V_{rms} = \frac{V_{max R}}{\sqrt{2}} = \frac{306.545}{\sqrt{2}} = 216.76 \text{ volts}$ Ans

Ans 3 b): Consider 6V source:

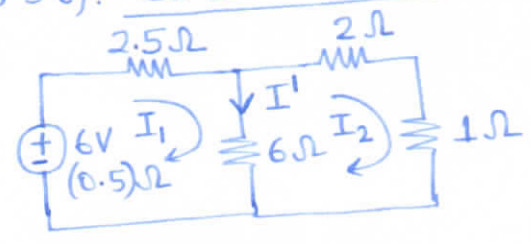

KVL equation of mesh - I

$$-0.5 I_1 + 6 - 2.5 I_1 - 6(I_1 - I_2) = 0$$

$$-9 I_1 + 6 I_2 = -6 \quad \text{--- (1)}$$

KVL equation of mesh - II


$$-6(I_2 - I_1) - 2 I_2 - 1 I_2 = 0$$

$$6 I_1 - 9 I_2 = 0 \quad \text{--- (2)}$$

solving eq. (1) & (2) we get,
 $I_1 = 1.2 \text{ A}$, $I_2 = 0.8 \text{ A}$

$\therefore I' = I_1 - I_2 = 1.2 - 0.8 = 0.4 \text{ A}$ (\downarrow)

Consider 12V source

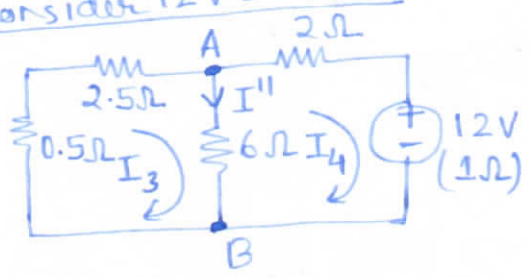

KVL equation of mesh - I

$$-0.5 I_3 - 2.5 I_3 - 6(I_3 - I_4) = 0$$

$$-9 I_3 + 6 I_4 = 0 \quad \text{--- (3)}$$

KVL equation of mesh - II

$$-6(I_4 - I_3) - 2 I_4 - 12 - 1 I_4 = 0$$


$$6 I_3 - 9 I_4 = 12 \quad \text{--- (4)}$$

solving eq. (3) & (4) we get,
 $I_3 = -1.6 \text{ A}$, $I_4 = -2.4 \text{ A}$

$\therefore I'' = I_3 - I_4 = -1.6 - (-2.4) = 0.8 \text{ A}$ (\downarrow)

Hence current in branch AB (6Ω) = $I' + I'' = 0.4 + 0.8 = 1.2 \text{ A}$ (\downarrow) Ans

Ans 4 a):

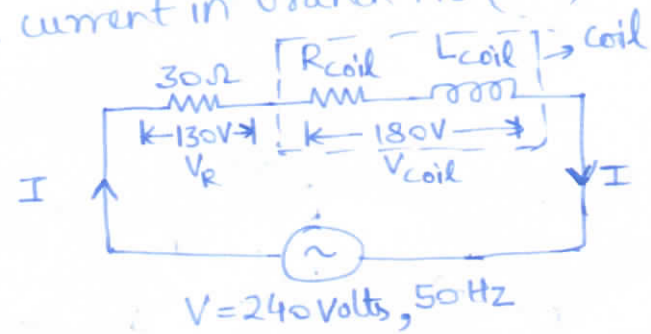

current in the circuit,


$$I = \frac{V_R}{30} = \frac{130}{30} = 4.33 \text{ A}$$

Now draw phasor diagram of the circuit:

In ΔOBC : $OC^2 = OB^2 + BC^2$

$$OC^2 = (OA + AB)^2 + BC^2$$
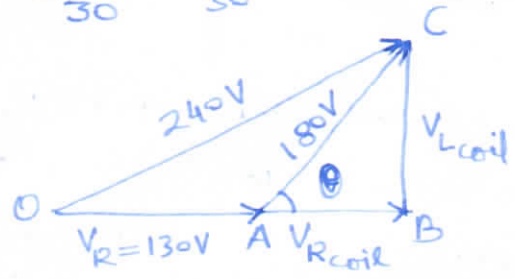
$$(240)^2 = (130 + 180 \cos \theta)^2 + (180 \sin \theta)^2$$



$$(240)^2 = (130)^2 + (180)^2 \cos^2 \theta + 2 \times 130 \times 180 \cos \theta + 180^2 \sin^2 \theta$$

$$(240)^2 = (130)^2 + (180)^2 (\cos^2 \theta + \sin^2 \theta) + 2 \times 130 \times 180 \cos \theta$$

$$(240)^2 = (130)^2 + (180)^2 + 2 \times 130 \times 180 \cos \theta$$

$$\cos \theta = \frac{83}{468} = 0.17735$$

$$\theta = \cos^{-1}(0.177) = 79.78^\circ$$

$$\therefore V_{R_{coil}} = 180 \cos \theta = 180 \times 0.177 = 31.92 \text{ volts}$$


$$\therefore R_{coil} = \frac{V_{R_{coil}}}{I} = \frac{31.92}{4.33} = 7.37 \Omega \text{ Ans}$$

$$V_{L_{coil}} = 180 \sin(79.78) = 177.14 \text{ volts}$$

$$X_{L_{coil}} = \frac{V_{L_{coil}}}{I} = \frac{177.14}{4.33} = 40.91 \Omega$$


$$\therefore L_{coil} = \frac{X_{L_{coil}}}{2\pi f} = \frac{40.91}{2\pi \times 50} = 130.22 \text{ mH} = 0.1302 \text{ H} \text{ Ans}$$

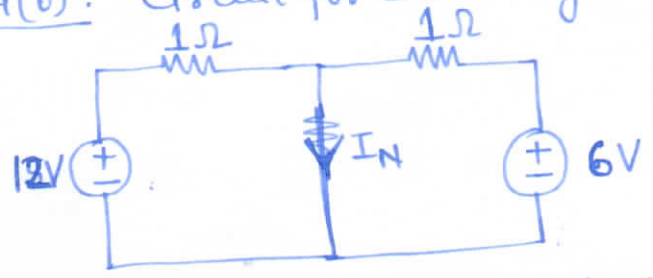Ans 4(b): Circuit for calculating I_N (Norton's current)




$$I_N = I_1 + I_2 = \frac{12}{1} + \frac{6}{1} = 18 \text{ A}$$

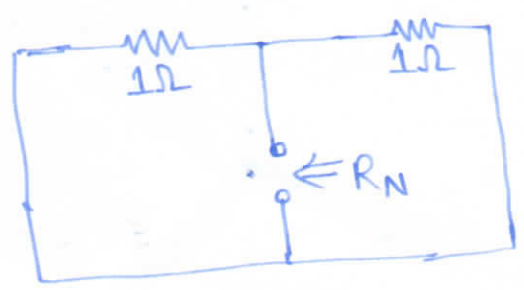Circuit for calculating R_N (Norton's resistance)



$$R_N = 1 \parallel 1 = \frac{1}{2} = 0.5 \Omega$$

Draw Norton's Equivalent circuit

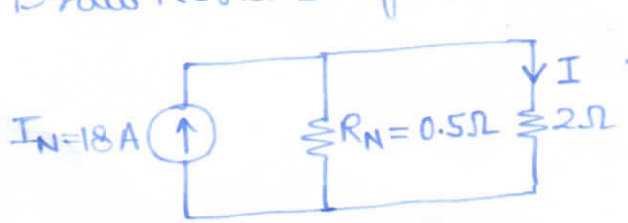

$$\therefore I = \frac{18 \times 0.5}{0.5 + 2} = 3.6 \text{ A} \text{ Ans}$$

Ans 5a): given $R = 2\Omega$, $L = 2\text{mH} = 2 \times 10^{-3}\text{H}$, $C = 10\mu\text{F} = 10 \times 10^{-6}\text{F}$ (6)

$$\text{resonant frequency } f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} = \frac{1}{2\pi} \sqrt{\frac{1}{2 \times 10^{-3} \times 10 \times 10^{-6}}} = 1125.39 \text{ Hz}$$

$$Q\text{-factor} = \frac{2\pi f_0 L}{R} = \frac{2\pi \times 1125.39 \times 2 \times 10^{-3}}{2} = 7.071 \text{ Ans}$$


$$\text{Bandwidth } (\Delta f) = \frac{R}{2\pi L} = \frac{2}{2\pi \times 2 \times 10^{-3}} = 159.15 \text{ Hz}$$

Half power frequencies,

$$f_1 = f_0 - \frac{R}{4\pi L} = 1125.39 - \frac{159.15}{2} = 1045.81 \text{ Hz}$$

$$f_2 = f_0 + \frac{R}{4\pi L} = 1125.39 + \frac{159.15}{2} = 1204.96 \text{ Hz}$$




Ans 5b):

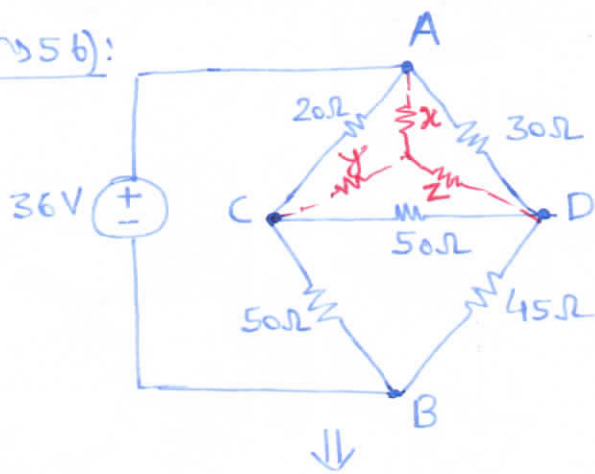

using delta to star conversion in network ADC,

$$x = \frac{20 \times 30}{20 + 30 + 50} = 6\Omega ; y = \frac{20 \times 50}{20 + 30 + 50} = 10\Omega$$
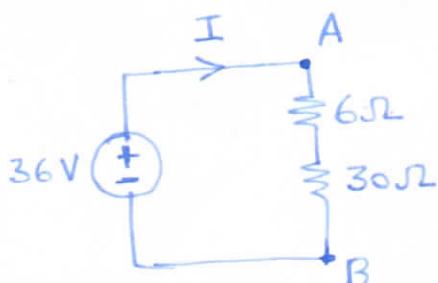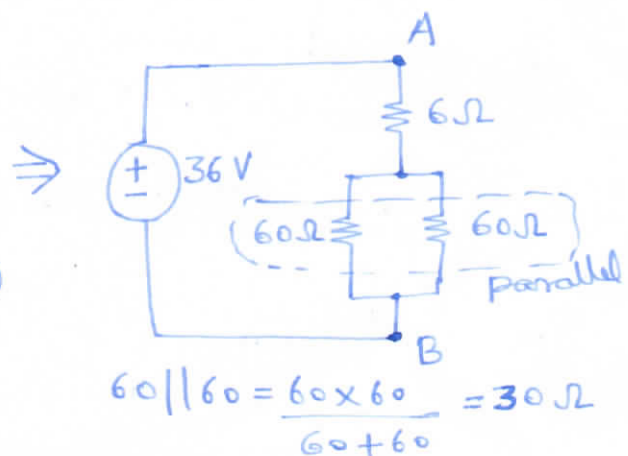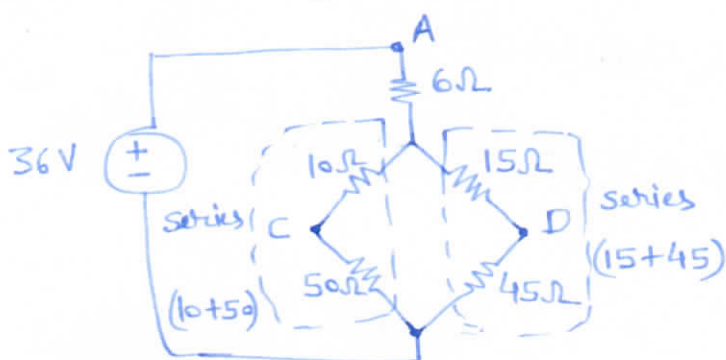
$$z = \frac{30 \times 50}{20 + 30 + 50} = 15\Omega$$



$$I = \frac{36}{6 + 30} = 1 \text{ A}$$