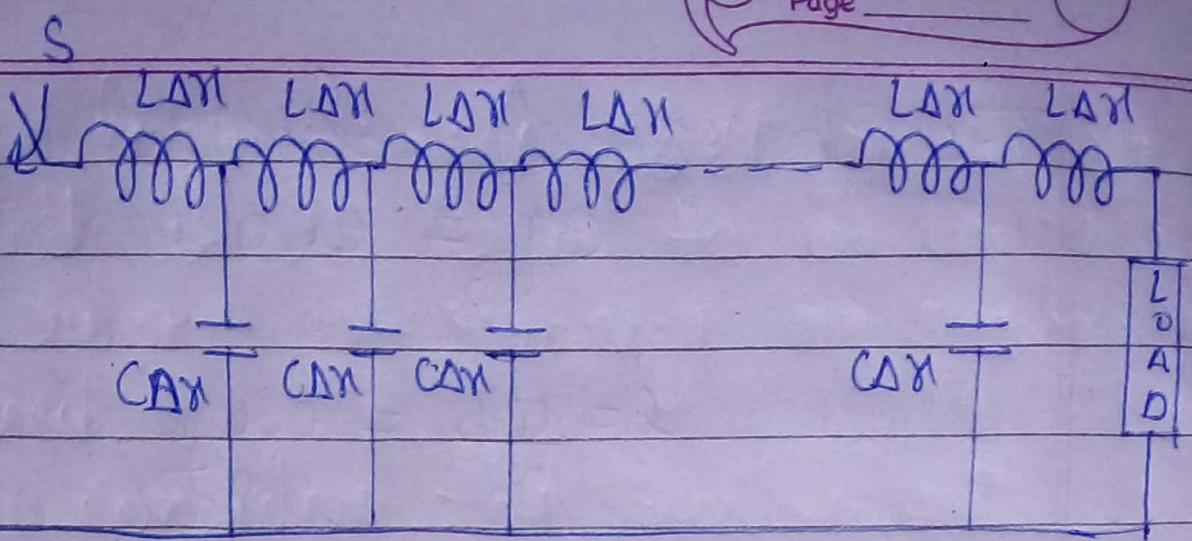


(2) A surge is a movement of charge along the conductor.

Consider a lossless transmission line which has series inductance (L_{SL}) of length Δx_1 & shunt capacitance (C_{SL}) of length Δx_2 .



When the switch S is closed, the current passing through the first inductor is zero because it acts as an open circuit.

It is therefore clear that the voltage at the successive section builds up gradually & finally the voltage wave reaches the other end of the line.

Wave equation-

$$\frac{\partial^2 e}{\partial x^2} = LC \frac{\partial^2 e}{\partial t^2}$$

$$\frac{\partial^2 i}{\partial x^2} = LC \frac{\partial^2 i}{\partial t^2}$$