

Proof - Let us assume 1ϕ transformer in which the total series imp. referred to primary is Z_{1e} , base current & voltage are I_1 & V_1 , respectively.

$$\therefore (Z_1)_{\text{base}} = Z_{b1} = V_1 / I_1 \quad \text{--- (1)}$$

$$(Z_1)_{\text{pu}} = \frac{Z_{1e}}{Z_{b1}} = \frac{Z_{1e} \cdot I_1}{V_1} \quad \text{--- (2)}$$

Also, total series imp. referred to secondary,

$$Z_{2e} = Z_{1e} \cdot (N_2 / N_1)^2 \quad \text{--- (3)}$$

$$Z_{b2} = \frac{V_2}{I_2} \quad \text{--- (4)}$$

$$(Z_2)_{\text{pu}} = \frac{Z_{2e}}{Z_{b2}} = \frac{Z_{2e} \cdot I_2}{V_2} \quad \text{--- (5)}$$

$$\therefore I_2 = I_1 \cdot N_1 / N_2$$

$$V_2 = \frac{N_2}{N_1} \cdot V_1$$

Hence, $(Z_2)_{\text{pu}} = Z_{1e} \left(\frac{N_2}{N_1} \right)^2 \cdot \frac{I_1 N_1}{N_2} \cdot \frac{N_1}{N_2 V_1}$

$$(Z_2)_{\text{pu}} = \frac{Z_{1e} \cdot I_1}{V_1}$$

$$(Z_2)_{\text{pu}} = (Z_1)_{\text{pu}}$$

proved

Numerical. -

Given that,

$$(MVA)_b = 30 \text{ MVA}$$

$$V_b = 11 \text{ kV}$$

$$X = 20\% = \text{or } 0.2$$

$$\therefore I_b = \frac{(MVA)_b}{V_b}$$

$$= \frac{30 \times 10^6}{11 \times 10^3}$$

$$= 2.73 \times 10^3$$

$$X_b = \frac{V_b}{I_b}$$

$$= \frac{11 \times 10^3}{2.73 \times 10^3}$$

$$= 4.033 \Omega$$

$$X_{pu} = \frac{0.2}{4.033} = 0.0496 = 0.05 \text{ pu}$$

for 50 MVA, 10 kV base we get,

$$(X_{pu})_{\text{new}} = (X_{pu})_{\text{old}} \cdot \frac{(MVA)_{\text{new}}}{(MVA)_{\text{old}}} \cdot \frac{(kV)_{\text{old}}^2}{(kV)_{\text{new}}^2}$$

$$= (0.05) \cdot \left[\frac{30}{50} \right] \cdot \left[\frac{11}{10} \right]^2$$

$$= 0.025 \text{ pu}$$