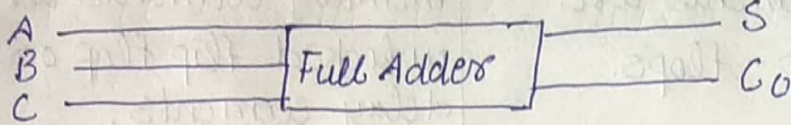


Q.2

Ans:-

Full adder:- Full adder is a circuit that performs the addition of three binary digits. It has three inputs A, B and C with two outputs S and Co, where C is the previous carry.



② if there are three input variables the combinations are eight ($2^3 = 8$). Now from the truth table of the full adder.

Inputs			Outputs	
A	B	C	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

For S

	BC	00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6

For Co

	BC	00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6

③ Sum: $S = ABC + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}C$

Carry!- $C_0 = AB + AC + BC$

④ A full adder can be implemented using two half adders and one OR gate.

Sum: $S = ABC + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}\bar{B}C$

$$= ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$= C(AB + \bar{A}\bar{B}) + \bar{C}(A\bar{B} + \bar{A}B)$$

$$= C(A\bar{B} + \bar{A}B)' + \bar{C}(A\bar{B} + \bar{A}B)$$

$$= (A \oplus B) \oplus C$$

Carry!- $C_0 = AB + AC + BC$

$$= AB + C(A + B)$$

$$= AB + C(A + B)(A + \bar{A})(B + \bar{B})$$

$$= AB + C[AB + A\bar{B} + \bar{A}B]$$

$$= AB + ABC + C(A\bar{B} + \bar{A}B)$$

$$= AB(1 + C) + C(A \oplus B)$$

$$= AB + C(A \oplus B)$$

