

Q.1

Section-05

Ans

A shift register than can shift the data in both the directions as well as load it parallelly, it is called as a universal shift register.

(2)

The shift register is capable of performing the following operations:-

- (i) Parallel loading.
- (ii) Left shifting.
- (iii) Right shifting.

(3)

The block diagram of a 4-bit universal shift register is shown.

(4)

The multiplexers have two common select lines S_1 and S_0 . Input I_0 in each multiplexer is selected when $S_1 S_0 = 00$.

(5)

The selection inputs (S_1, S_0) controls the mode of operation of the registers according to the function table shown.

S_1	S_0	Function
0	0	Hold
0	1	Shift Right
1	0	Shift Left
1	1	Load

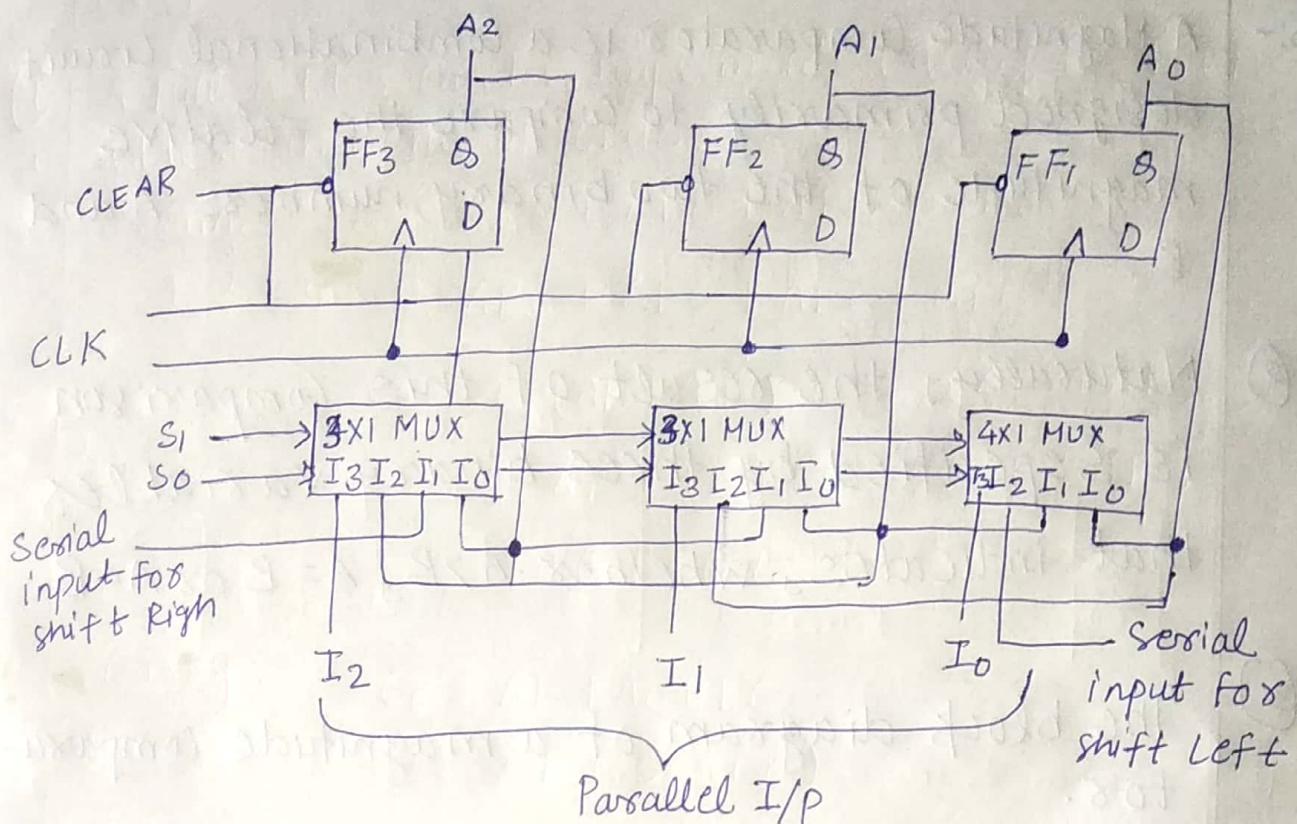


diagram:- universal shift Register.

Operations:-

- ① when $S_1, S_0 = 01$, the input I_1 of the Multiplexer has a path to the D inputs of the flip flops. this causes a shift right operation, with the Serial input transferred in flip flop FF4.
- ② When $S_1, S_0 = 11$, the binary information on the parallel input lines is transferred into the registers simultaneously during the next clock edge.