

XOR gate in an inverter.

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

Figure above shows the truth table of a 2-input XOR gate. It has two input A, B and one output out. On looking we observe that:

- If one of the inputs (say B) is 0, out is equal to the other input. For instance when $B = 0$

- out = 0 when $A = 0$

- out = 1 when $A = 1$

Similarly if one of the inputs is 1, out is equal to inverse of the other input.

For instance, when $B = 1$

out = 1 when $A = 0$

out = 0 when $A = 1$

Using the information, XOR gate can be easily converted to an inverter.

Inverter design using XOR gate: Similarly

We can realize an inverter using XOR gate by connecting one of the inputs to logic 1. As shown in the truth table below

A	B	Out
1	0	1
1	1	0

