

Ques 1:- Explain Multi stage transistor in brief.

In Multi-stage amplifiers, the output of first stage is coupled to the input of next stage using a coupling device. These coupling devices can usually be a capacitor or a transformer. This process of joining two amplifier stages using a coupling device can be c/d as cascading.

They are used to boost very weak signals to usable levels.