


Ans (6)

b) Norton's theorem


This theorem is used where it is easier to simplify a network in terms of current instead of voltages. This theorem reduces a normally complicated network to a simple parallel circuit consisting of

a) an ideal current source  $I_N$  of infinite internal resistance

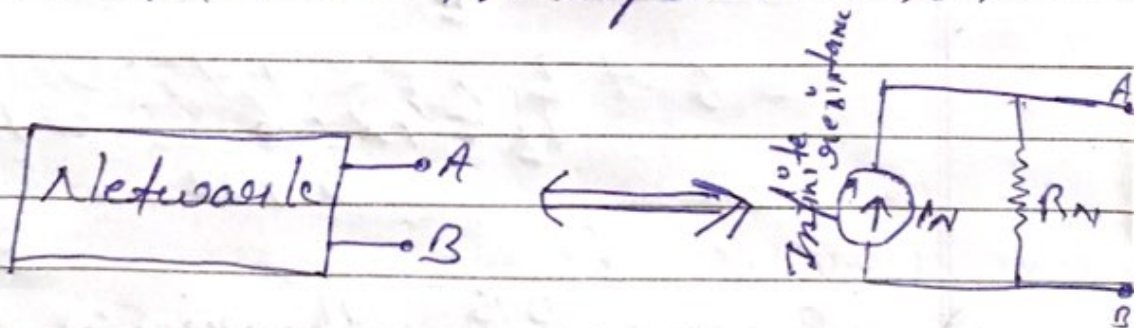b) a resistance  $R_N$  in parallel to it




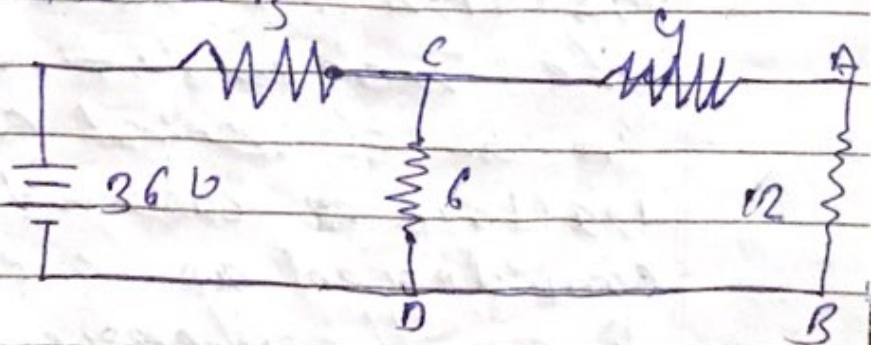Example. using Norton theorem find current in  $2\ \Omega$




$$= 3 + 6 \parallel 4 = 3 + 2.4 = 5.4 \Omega$$
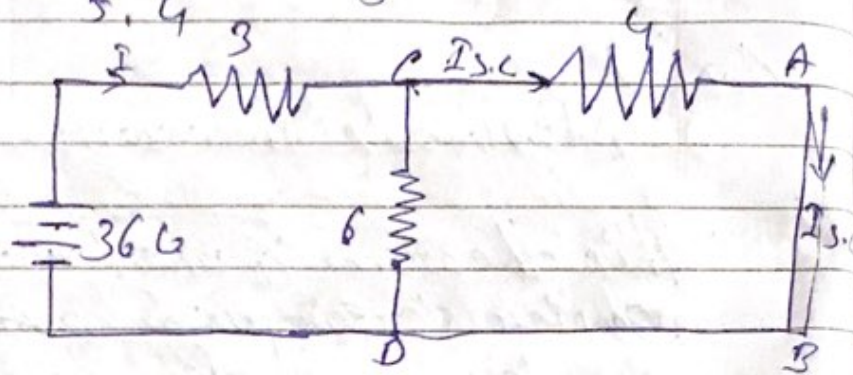
$$I = \frac{36}{5.4} = \frac{20}{3} \text{ A}$$



$$I_{s.c} = \frac{20}{3} \times \frac{6}{10} = 4 \text{ A}$$

$$= 4 + 6 \parallel 3 = 6 \Omega$$

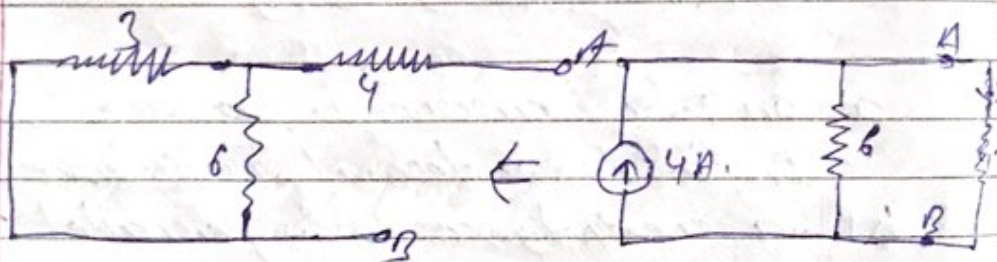


$$I_2 = 4 \times \frac{6}{6 + 12} = 1.33 \text{ A}$$

a) Superposition theorem :-)

The superposition theorem is a method for the independent supplies present in an electrical circuit like voltage & current and that is considered as one supply at a time. The theorem tells that

In a linear n/w comprising one or more sources, the flow of current through a number of supplies in a circuit is the algebraic calculation of the current when acting the sources like independently.

Example

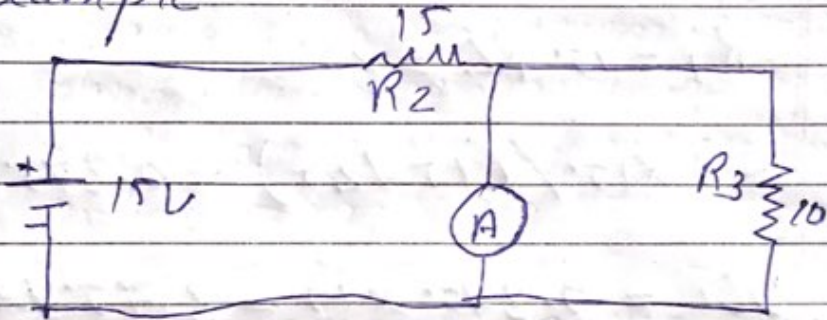

$$V_L = V_S \cdot (R_3 / (R_3 + R_2))$$


$$V_S = 15, R_3 = 10 \text{ \& } R_2 = 15$$


$$V_{L1} = V_S = R_3 / (R_3 + R_2)$$

$$15 (10 / (10 + 15))$$

$$15 (10 / 25)$$

$$= 6 \text{ Volts}$$

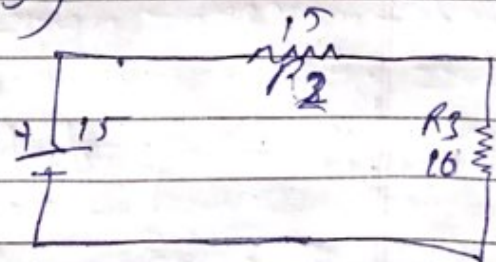

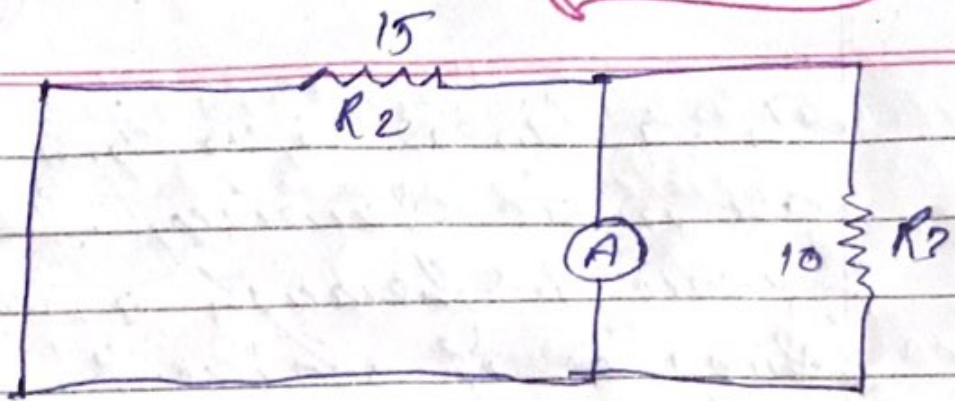

$$V_{L2} = I \times R$$

$$I_L = I \times R_1 / (R_1 + R_2)$$

$$R_1 = 15 \quad R_L = 10$$

$$= 1 \times 15 / (15 + 10) = 0.375 \text{ Amps}$$

$$V_{L2} = 0.375 \times 10 = 3.75 \text{ Volts}$$

$$\therefore V_L = V_{L1} + V_{L2}$$

$$= 6 + 3.75 = 9.75 \text{ Volts}$$