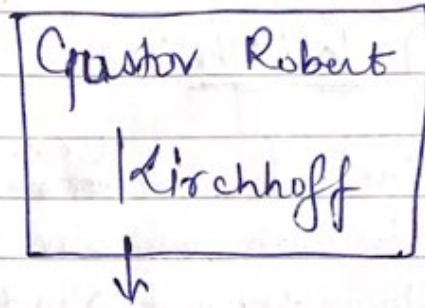


Ques 10:- Kirchhoff's Law:-

Answer.

→ Derived by :-




Extension of ohm's law.

① Kirchhoff's 1st law or (KCL):-

States that, in any network of conductors, the algebraic sum of currents meeting at a point is zero or the sum of incoming currents towards any point is equal to the sum of outgoing currents away from that point.

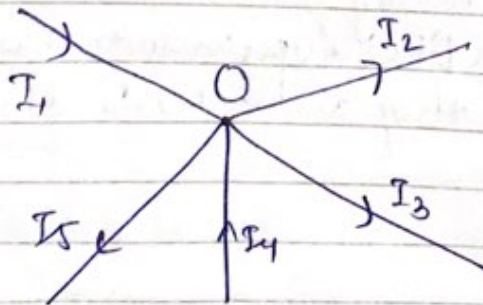Let, I_1, I_2, I_3, I_4 & I_5 meet at O, flow in directions shown by arrow:



Taking Incoming I as \oplus & outgoing as \ominus , then, from KCL:-

$I_3 R_3$ is \oplus ve (Rise in pot.ⁿ)
 $I_4 R_4$ is \ominus ve (fall in "
 E_2 is \ominus ve (fall in "
 E_1 is \oplus ve (Rise " "

from KVL :-

$$-I_1 R_1 - I_2 R_2 + I_3 R_3 - I_4 R_4 - E_2 + E_1 = 0$$

$$\text{or, } I_1 R_1 + I_2 R_2 - I_3 R_3 + I_4 R_4 = E_1 + E_2$$

